


Computer Electronics

Lecture 6: Digital Circuits and Verilog

Recap: Digital circuits


- Combinational (no feedback paths)
- Sequential (with feedback paths – remembers the past)
 - Asynchronous (no clock signal)
 - Synchronous (with clock signal)
- Asynchronous circuits
 - Very difficult to design: need to account for physical propagation delays and logic glitches
 - Only small designs: latches and flip-flops
- Synchronous circuits
 - Easy to design: propagation delays and glitches are forced out of the equation
 - During the clock period we wait for them to go away!
 - Really large designs: CPUs, GPUs, FPGAs, custom

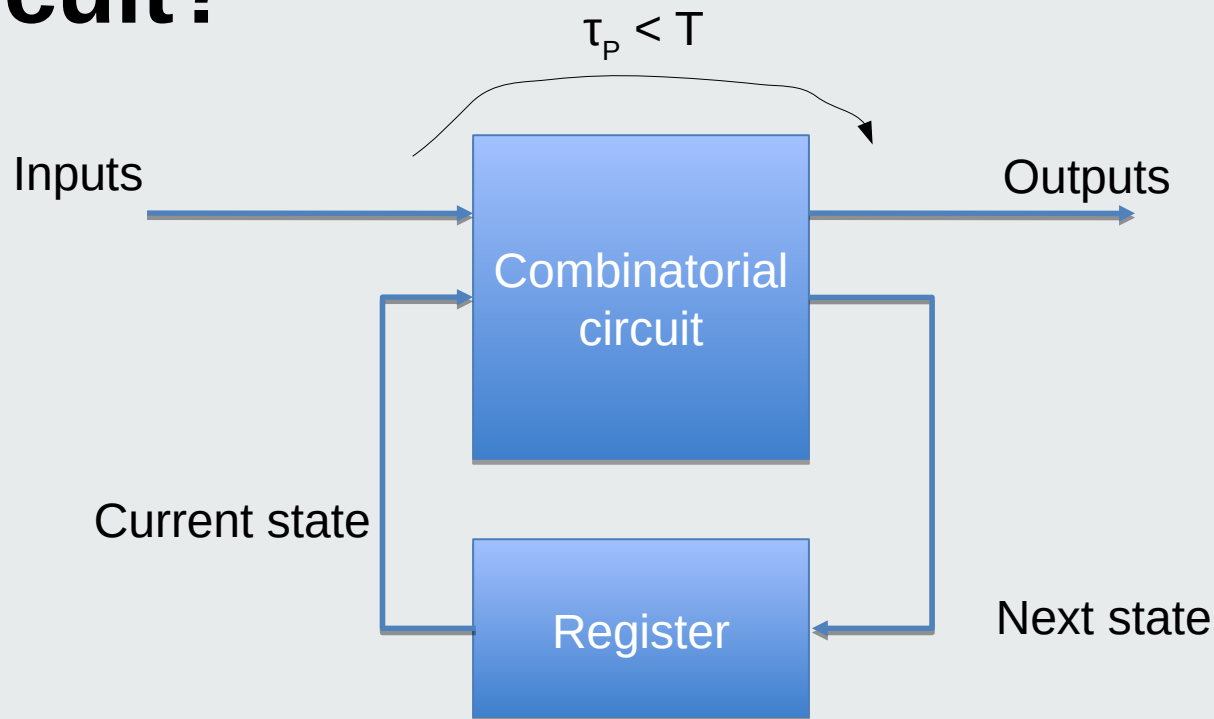Recap: what is inside of a digital circuit?



Recap: what is a combinatorial circuit?

 - Full adder circuit
- $S_i = S_i(a_i, b_i, c_i)$;
- $C_{i+1} = C_{i+1}(a_i, b_i, c_i)$




Propagation
delays!

Glitches!

Recap: what is a register


- It is a set of memory elements (flip-flops or latches)
- **Latches** are *transparent*, the output changes with the input if enabled: **RARELY USED**
- **Flip-flops** are *not transparent*, the output only changes at on of the active clock signal edge: **THEY ARE EVERYWHERE**

The FLIP-FLOP!

 

- Only D type is studied
- Verilog description is directly mapped to a library component
- Set (S) and Reset (R) are optional
- It is rare that S and R are simultaneously supported: no library component
- Responds to the rising (positive) edge of the clock (CLK)
- Responds to the falling (negative) edge of the clock if an inverter is placed at the CLK input (DANGER ZONE!)
- The optional Enable signal (EN) determines whether the flip-flop will respond or not to the clock edge

The FLIP-FLOP Timing Diagram

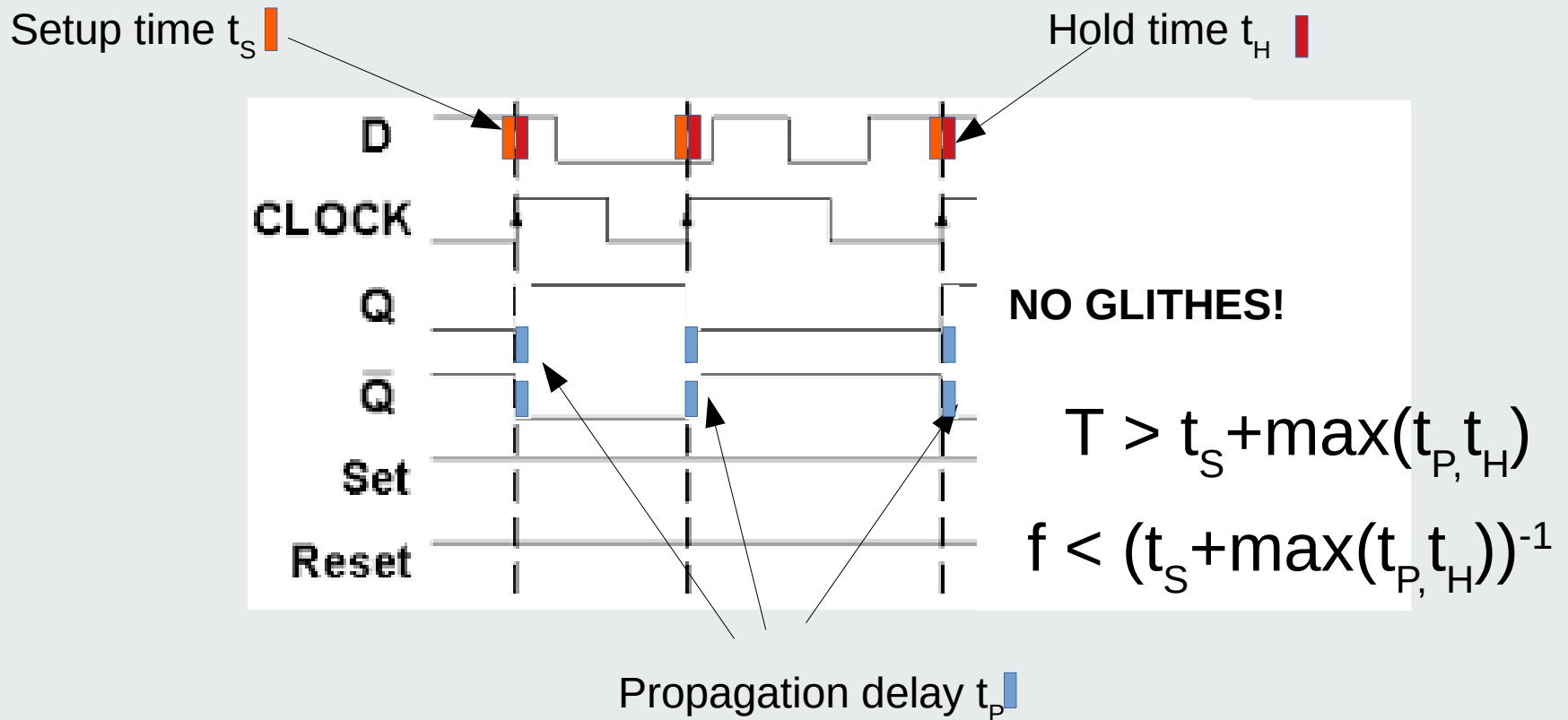


Behaviour summary

- The output Q takes the value of the input D at the active clock edge after time t_p
- The input D must be stable for at least a time t_s before the clock edge
- The input D must be stable for at least a time t_H after the clock edge (automatically guaranteed by propagation time)
- Violations of t_s and t_H result in malfunction!


The Flip-flop Set/Reset types

- Asynchronous
 - Output Q responds IMMEDIATELY (after small t_p) to assertions of S and R
- Synchronous
 - Output Q responds to S/R assertions present before the clock edge (before t_s)

The FLIP-FLOP with asynchronous reset

 

 
The FLIP-FLOP with synchronous reset and enable



So let's learn Verilog! Or NOT!

- The **iob-lib** repo has gone public as of today!
- The **iob-lib** repo contains
 - Useful Verilog macros to avoid writing the same Verilog description over and over again
 - Useful components (modules) to avoid writing the same Verilog description over and over again
- Enjoy!

Just learn 2 things!

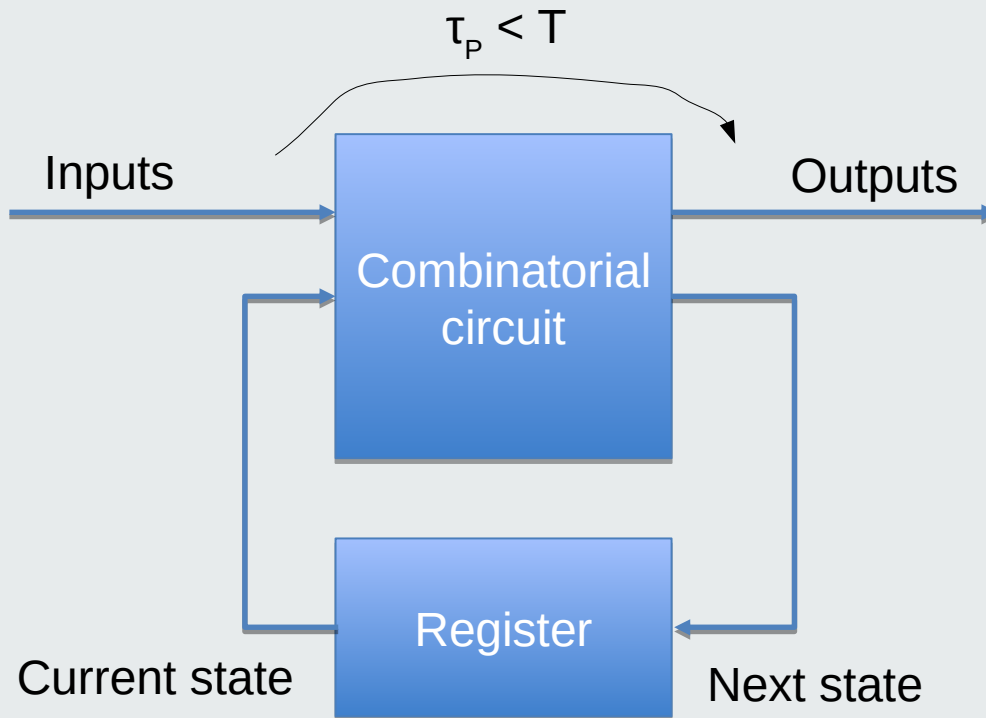

- If any digital circuit is just this then you just need to learn to describe:
 - combinatorial circuits
 - registers
- Not bad, is that?

Signal Wires

- Verilog describes circuits
- Circuits are blocks connected by wires that carry digital signals (0 or 1)
- So we need to declare and use wires
- Verilog describes two types of wires: *wire* and *reg*
- And the mess begins:
 - A *wire* is a wire but it cannot be used in all situations
 - A *reg* is a wire (not a register as the name suggests) but it cannot be used in all situations
- What a start!!!

wire versus reg

- So when do we use wire?
 - A component output must be a wire
 - The left hand side of an assign statement must be a wire
 - A resolved signal must be a wire
- So when do we use reg?
 - In the left hand side of expressions inside a process
- So what is assign, resolved signal, process?
- It's a long story to be made short with **iob-lib!**