

Computer Electronics

Lecture 9: Dedicated Processors

Why design a dedicated processor

- Not needed for anything else
- No or limited programmability needed
- Can reduce cost in volume production
- Can reduce power/energy consumption
- Better *form factor* (size matters)
- Has a simpler user interface


Dedicated processors combined with GPPs

- PCIe cards
- Graphics cards
- Surveillance equipment
- Audio equipment
- Etc.



Design of dedicated processors

- Data and control paths

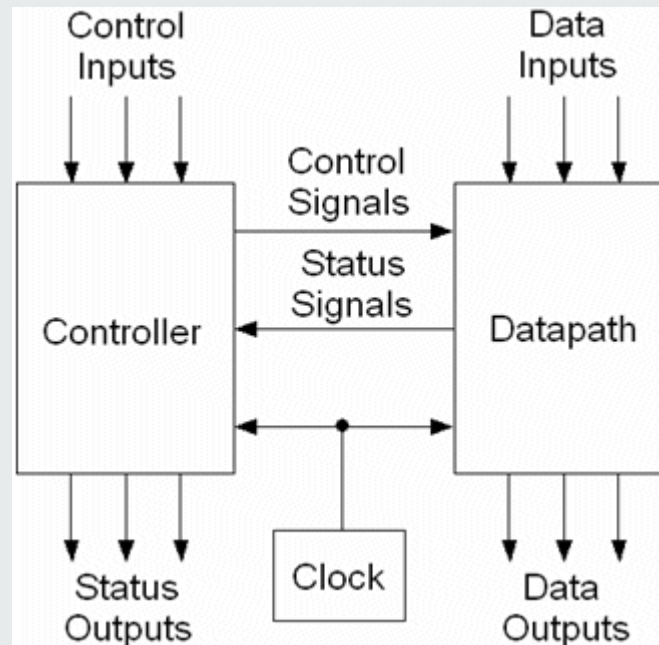


The Art of Design

- Describe the algorithm in a high-level text description
- Draw the datapath
- Write the pseudo-code for the control path (normally a FSM)
- Make sure you list:
 - IO signals: name, width, direction (I,O,IO), description
 - Registers: name, address, direction (Read, Write, RW), description
 - Memories: name, function (instructions, data, ..), volatile/non volatile, type (ROM,EPROM,RAM,reg file), internal/external, ports (single, dual, two-port, dual-port)
 - Holy Grail of Computing: N-port memory!!
 - Data streams: name, description, width, continuous/interrupted
 - Buses: name, purpose, type (Native, AXI, Wishbone, ISA, ...)
- Draw timing diagrams (use wavedrom, simulation of small circuits)


Design example: dedicated processor that computes p^q

- p is a streaming input (*volatile in C language*)
- Textual description already given
- Many possible architectures
- Many possible trade-offs...
- Let's get to the block diagram

Parallel architectures

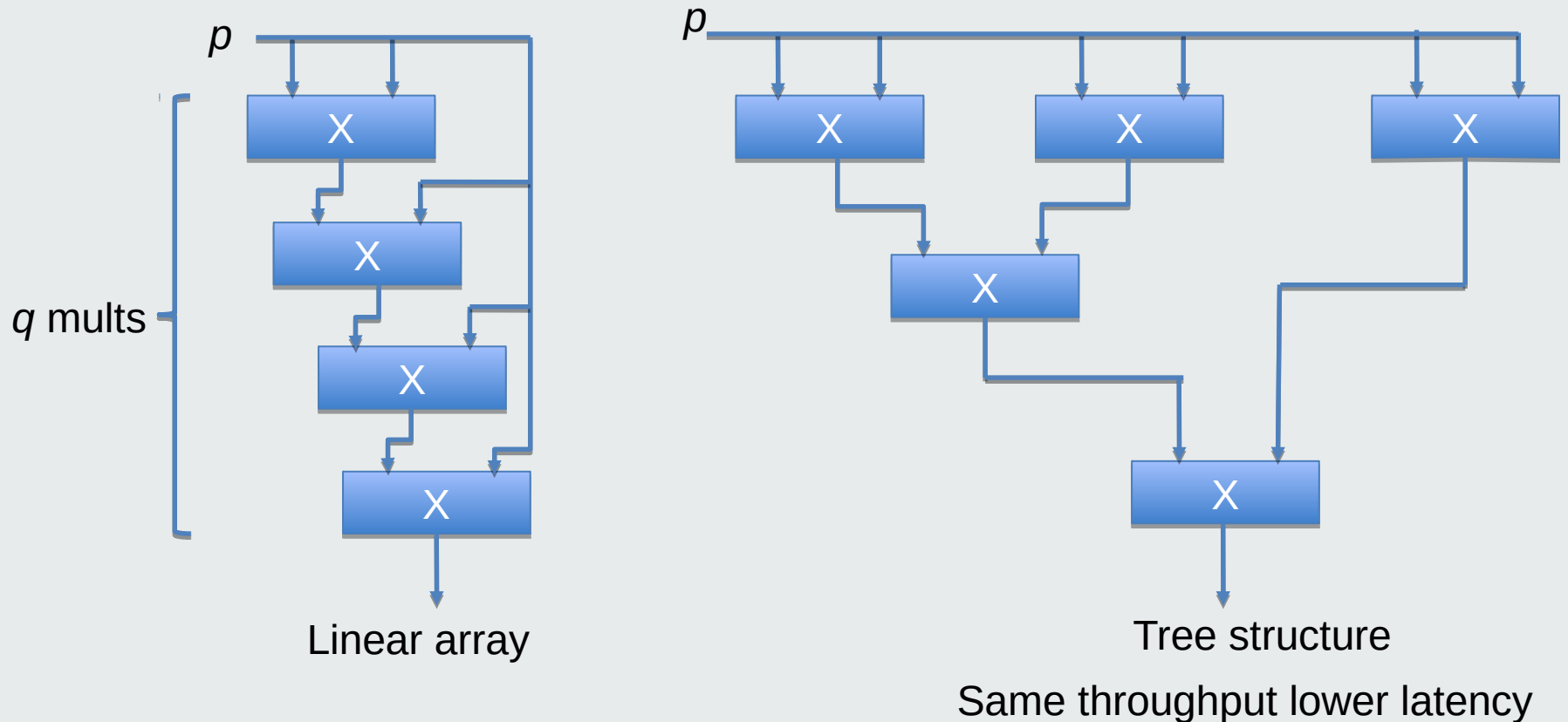


Data valid signals

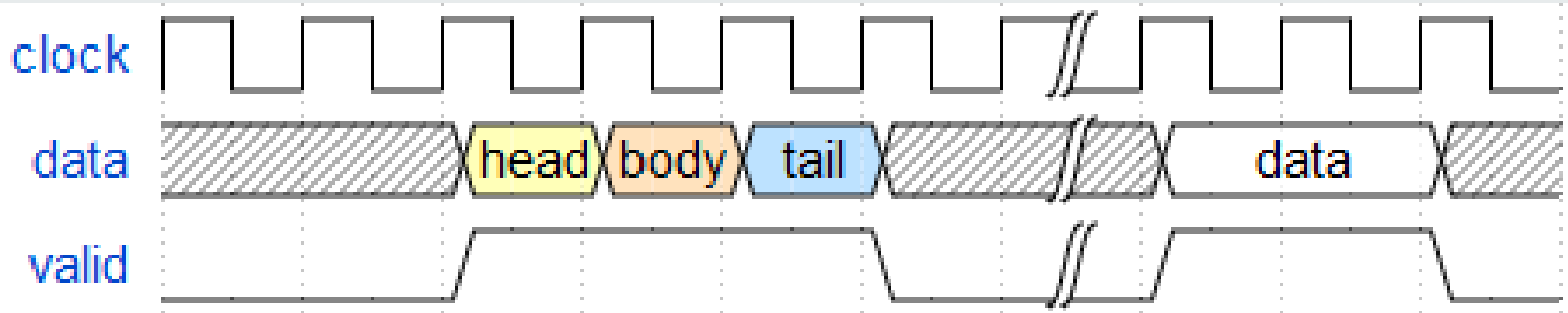

Interesting online tool: <http://wavedrom.com/editor.html>


Propagation of the **valid** signal

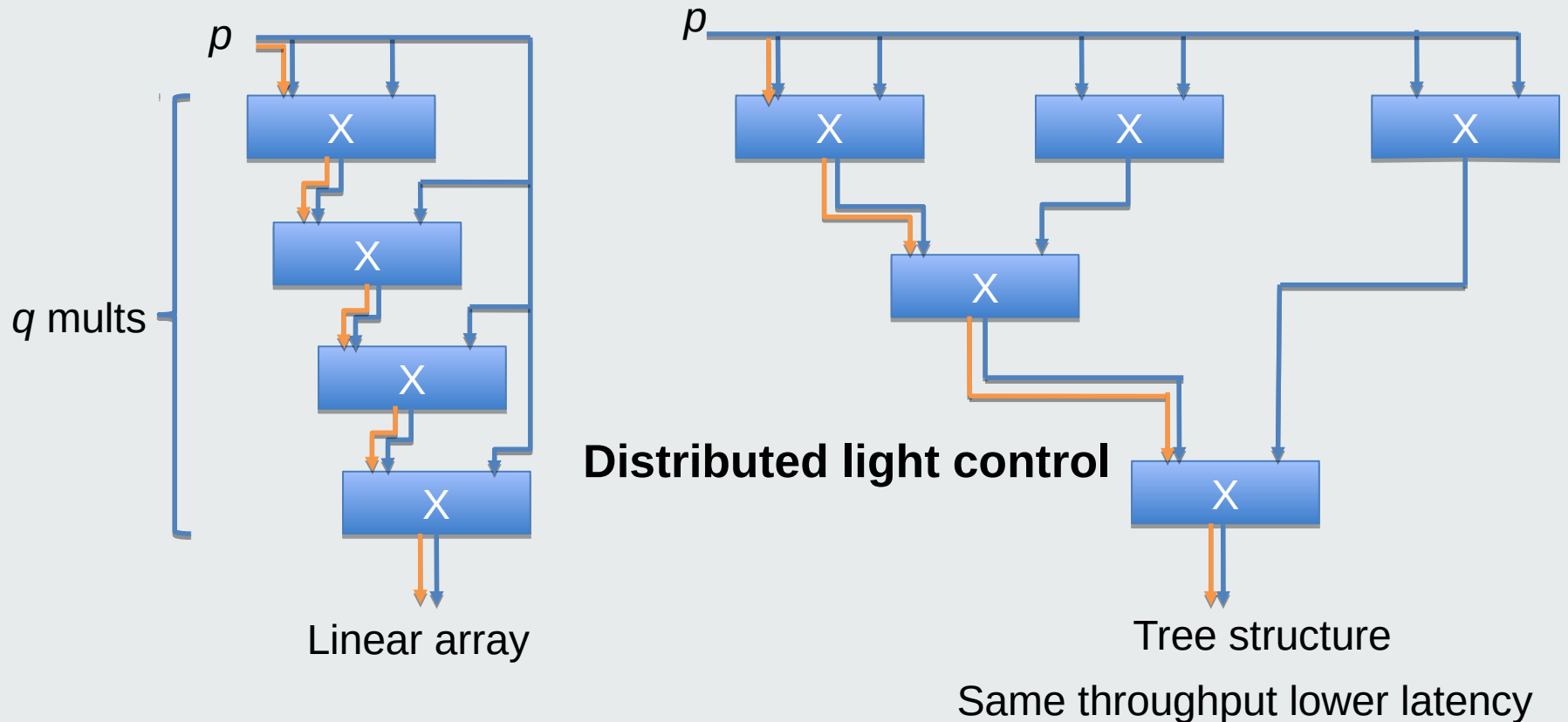

Parallel architecture: software accessible registers

- Register p : write-only, 16 bits for example
- Register q : write-only, 16 bits for example
- Register r (result): read-only, 32 bits for example
- Result comes fast: start and done registers may be dispensed with

Serial architecture: block diagram

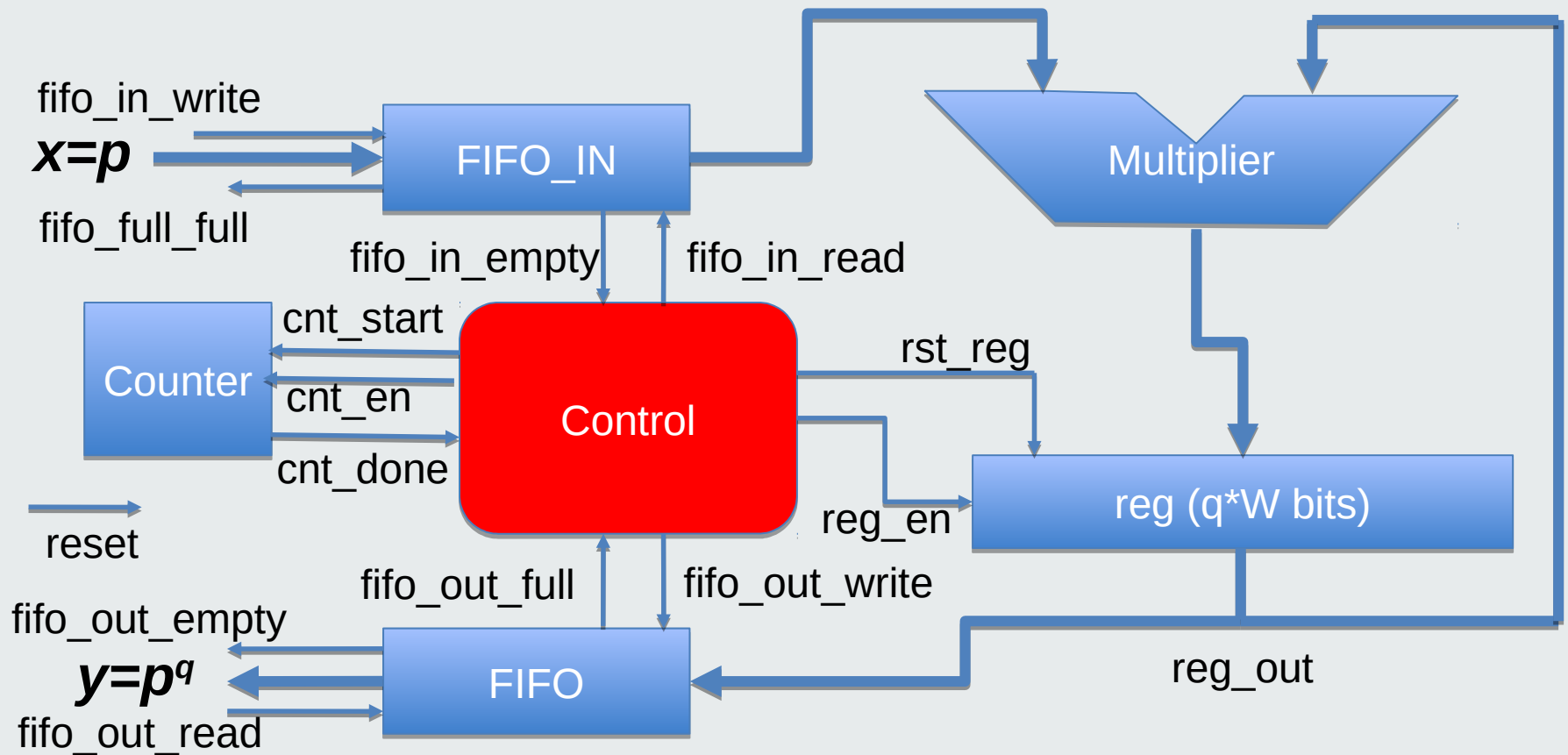


Serial architecture: software accessible registers

- Register p : write-only, 16 bits for example
- Register q : write-only, 16 bits for example
- Register r (result): read-only, 32 bits for example
- Result comes several clock cycles later, especially if q is large:
 - Start (1 bit, write-only) and Done (1 bit, write-only) registers are advisable
 - Alternatively, the timer can be used to wait for exactly the time the calculation will take


Design control circuit

- Flowchart ... better for software
- State transition diagram or table
- Pseudo-code
- Experienced designer: HDL (Verilog, VHDL, etc)

Controller canonical form

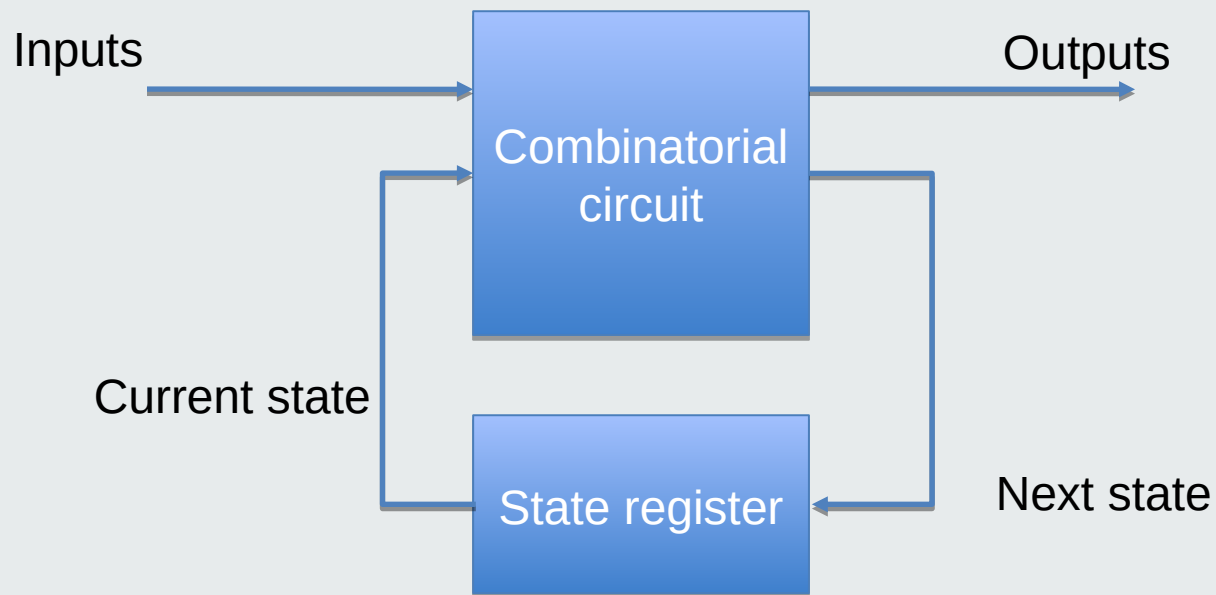

State transition diagram

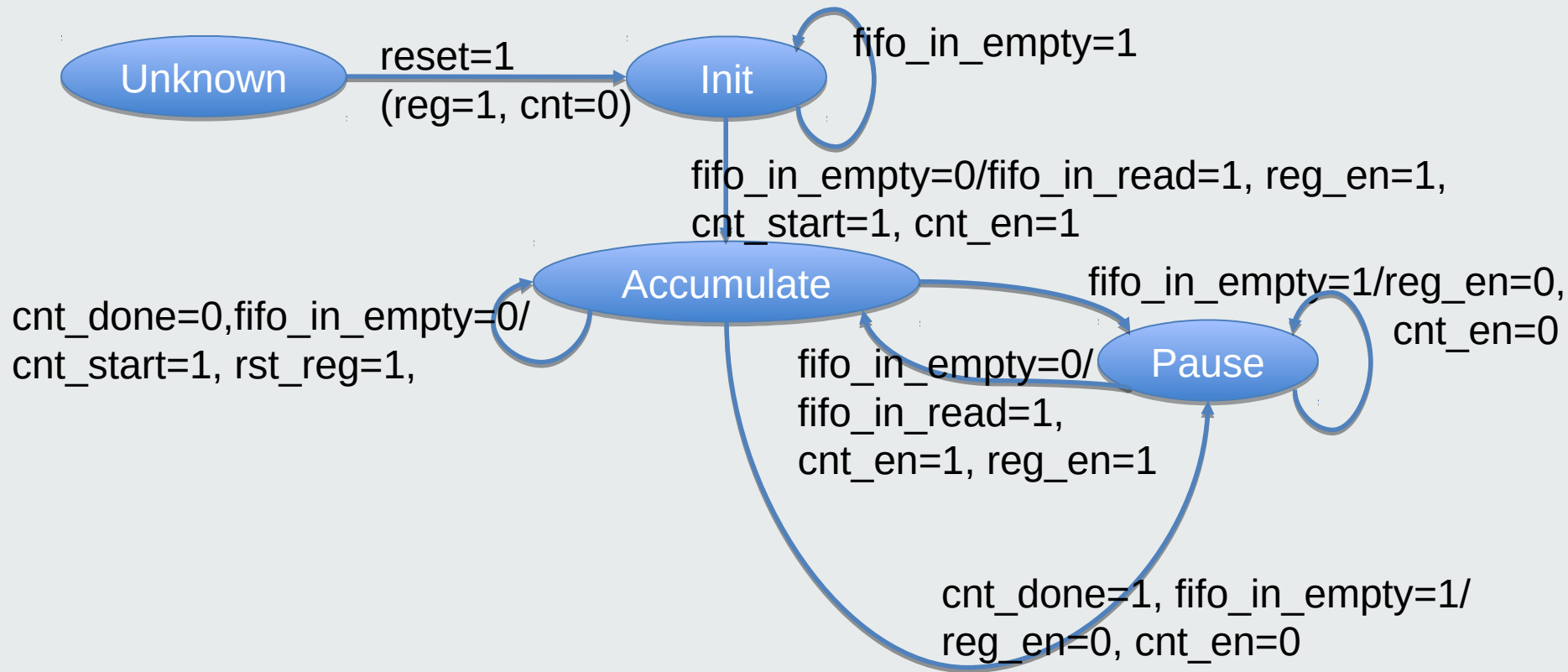

State transition table (very incomplete... no space!)

state	Inputs				Outputs			Next state
st	reset	cnt_done	fifo_in_empty	fifo_out_full	fifo_in_read	fifo_out_write	Reg_en	nxt_st
?	1	-	-	-	-	-	-	init
Init	0	0	1	0	0	0	0	init
Init	0	0	0	0	1	0	0	Accumulate
Accumulate								

Write finite state machines that look like assembly programs!

This program or FSM does not work,
only good for teaching \Rightarrow

```
`SIGNAL(pc, 3)
`SIGNAL(pc_next, 3)
`REG_AR(bclk, rst_bclk, 3'b0, pc, pc_next)

`COMB begin

    //default assignments
    pc_next = pc+1'b1;

    rst_reg = 1'b0;
    start_counter = 1'b0;
    en_counter = 1'b0;
    ...

case(pc)

    0: if (!START) begin //wait for sw start
        pc_next = pc;
    1: if (fifo_in_empty)
        pc_next = pc;
        else begin
            rst_reg = 1;
            start_counter = 1;
        end
    2: begin
        en_reg = 1;
        en_counter = 1;
    3: if (counter != q)
        pc_next <= 1;
    default: begin
        pc_next <= pc;
        done <= 1;

    endcase;

end // `COMB
```

Next steps

- Write HDL code (say Verilog) and simulate
- Run synthesis
 - Compiles Verilog and produces a generic netlist (gates and flip-flops not related to any technology)
- Run mapping
 - Converts generic netlist into technology dependent netlist using a component library
- Run place and route
 - Places cells and wire connections into layout
- If user time constraint violations tweak design or tool options and rerun
- Complex tools: full configuration requires scripting (in tcl normally)
- A competent designer or design manager can earn a few hundred K/year