


Computer Electronics

Lecture 18: Multiplier Circuits – Part 1


Lecture outline

- Parallel unsigned multiplier
- Parallel carry-save multiplier
- Signed multiplier
 - Subtraction review
 - Parallel signed multiplier

Unsigned matrix multiplier: algorithm

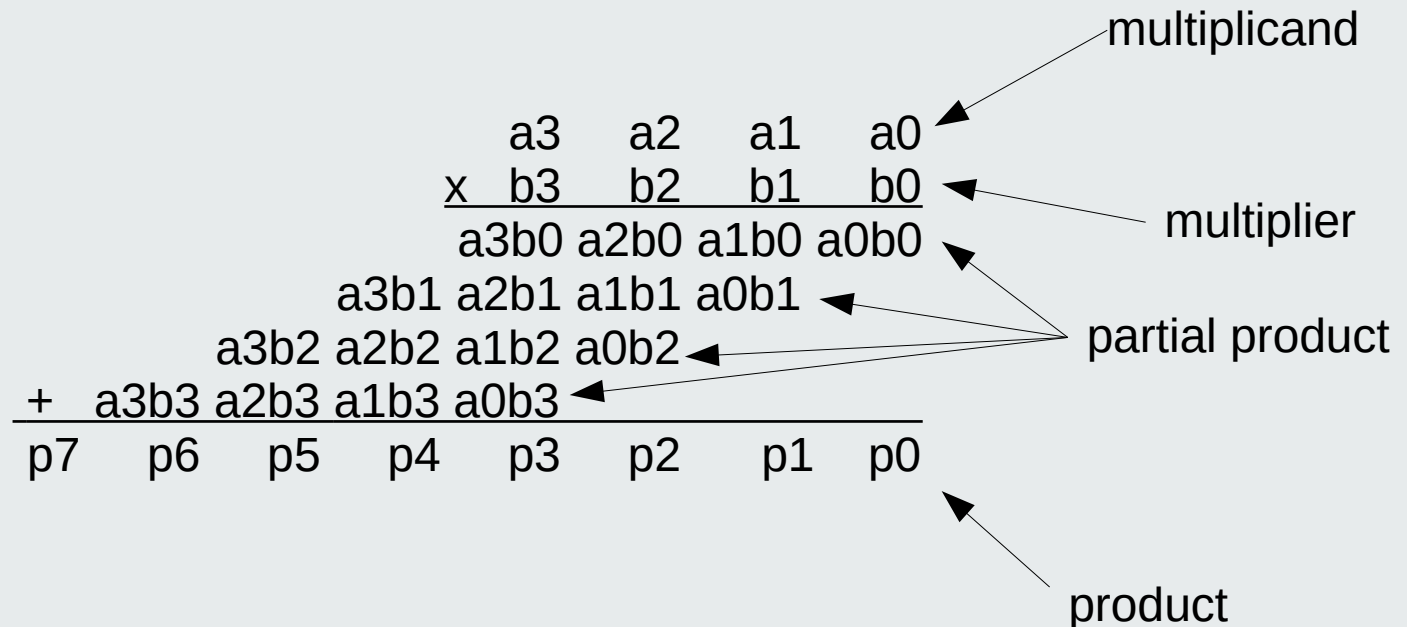

Matrix multiplier with ripple carry

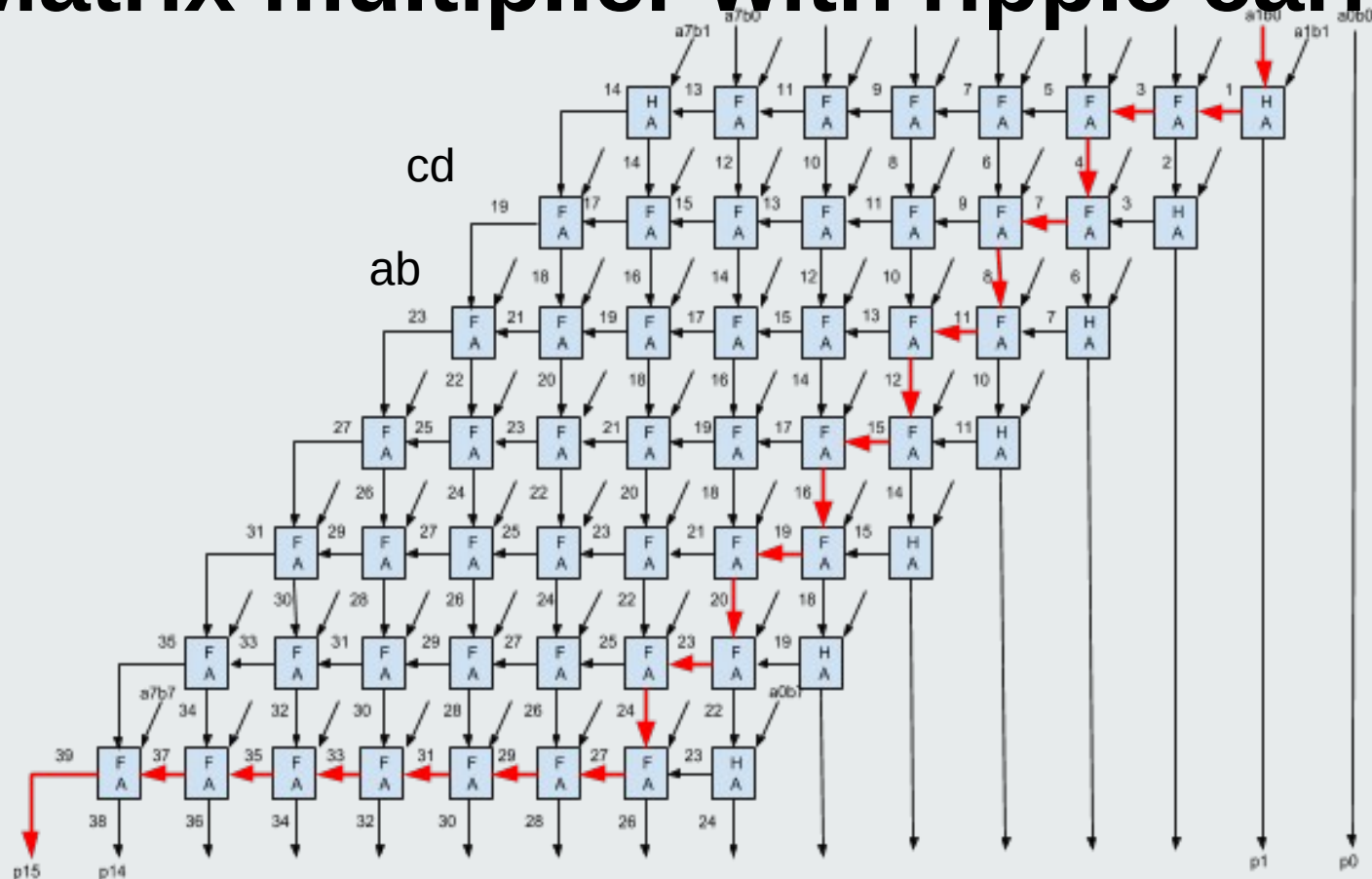


Pipelined MM w/ RCA


- Pipeline stages after each partial product addition
- What is the maximum clock frequency?

Carry-Save Adder Principle


Ripple-carry
adder

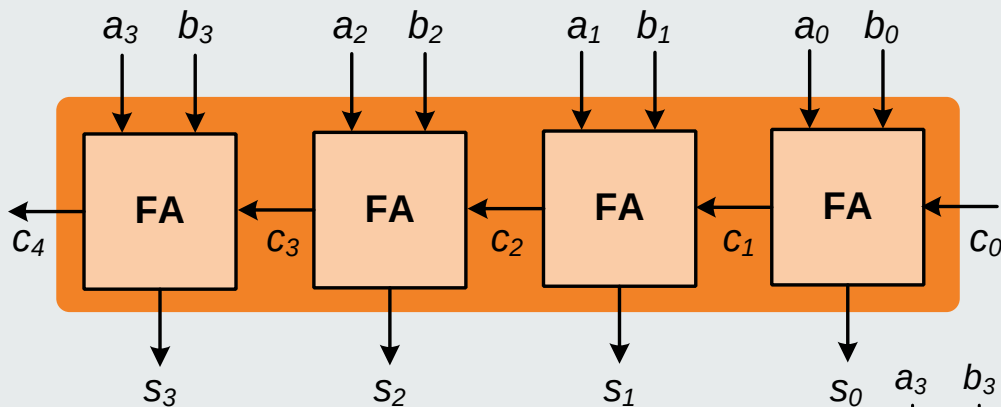


Carry-save
Adder stage

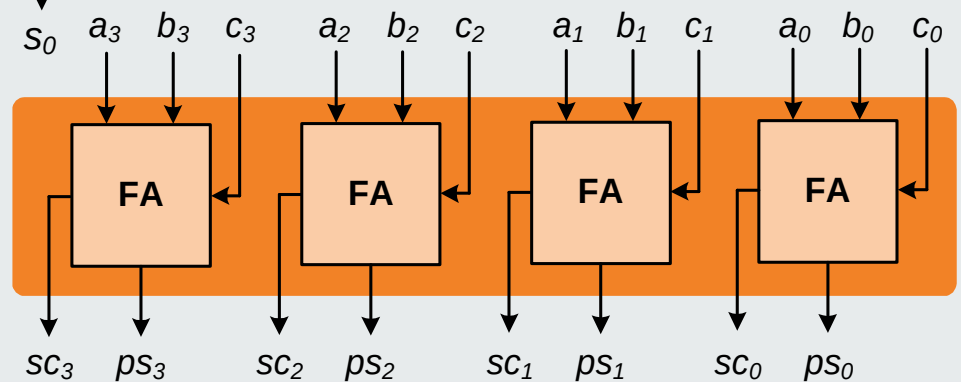

3-input adder using carry-save stage

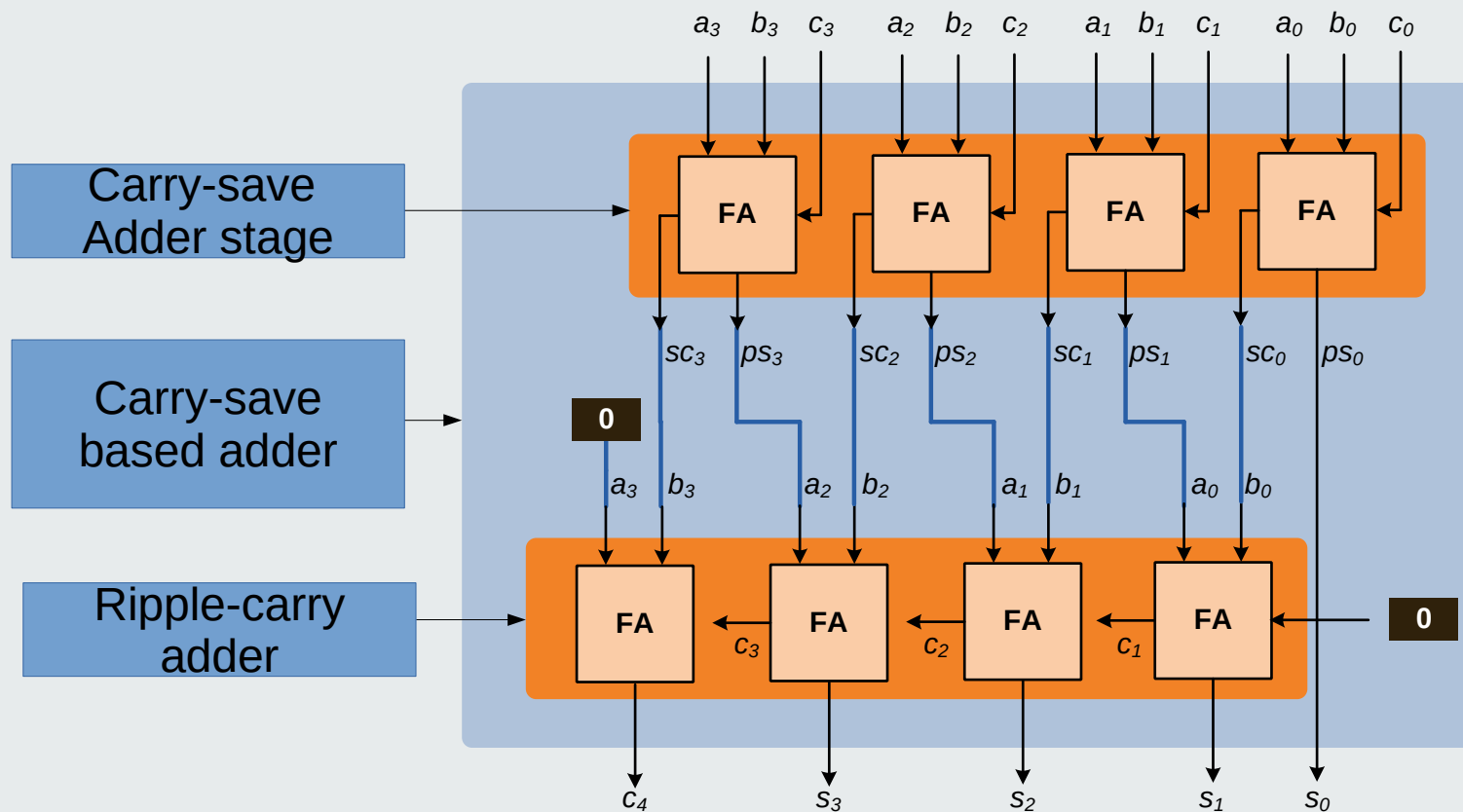

Matrix multiplier with carry save

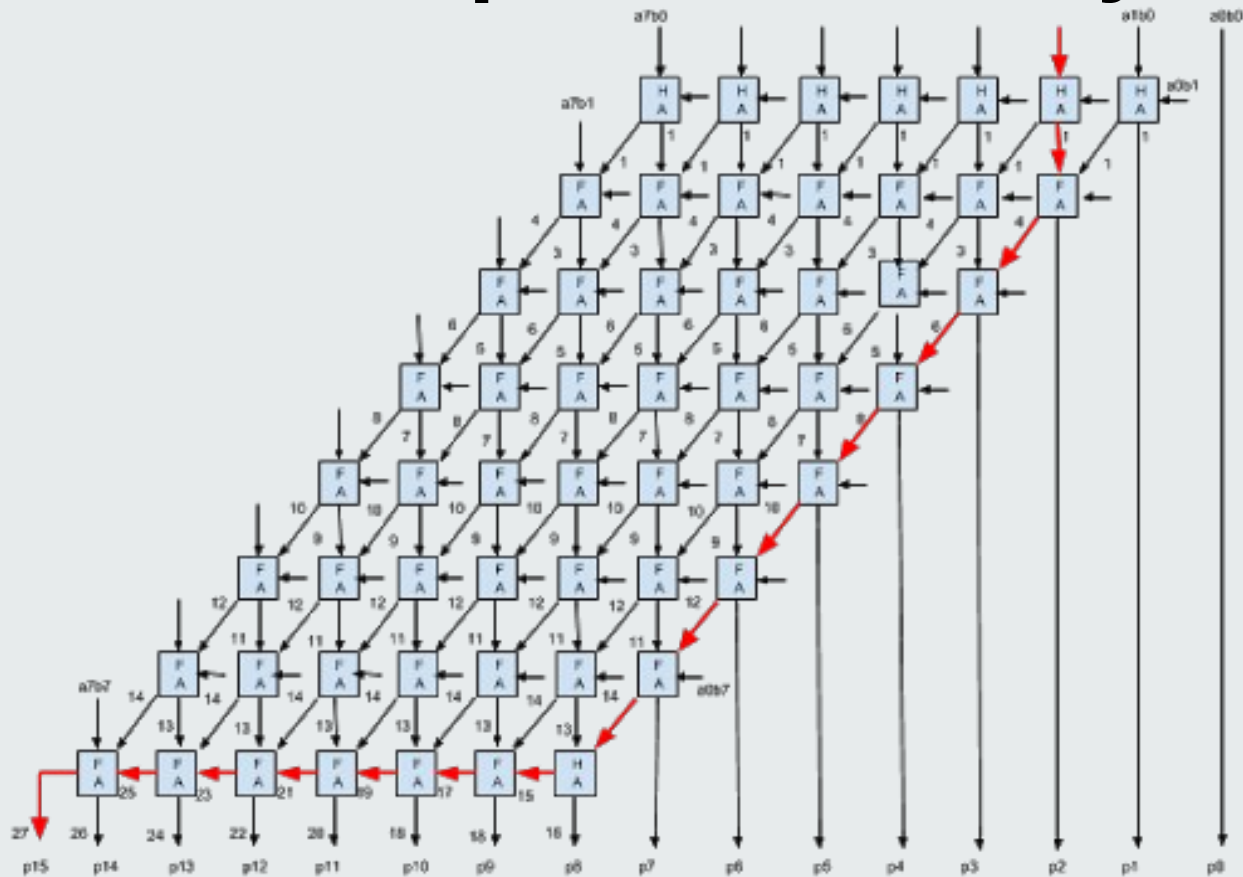


Pipelined MM w/ CSaA

- Pipeline stages after each partial product addition
- What is the maximum clock frequency?
 - What is the stage responsible for it?
- Solution for increasing the frequency
 - Work at the CSaA clock frequency
 - Use $N-1$ clock cycles to compute the last stage

Subtraction: fundamentals

- Adder circuits work equally well with unsigned and signed numbers
- $A - B = A + (-B)$
 - To subtract simply add the symmetric
 - Symmetric is 2's complement
 - Easiest way to compute 2's complement in hardware
 - Complement and add 1

Subtraction: circuit

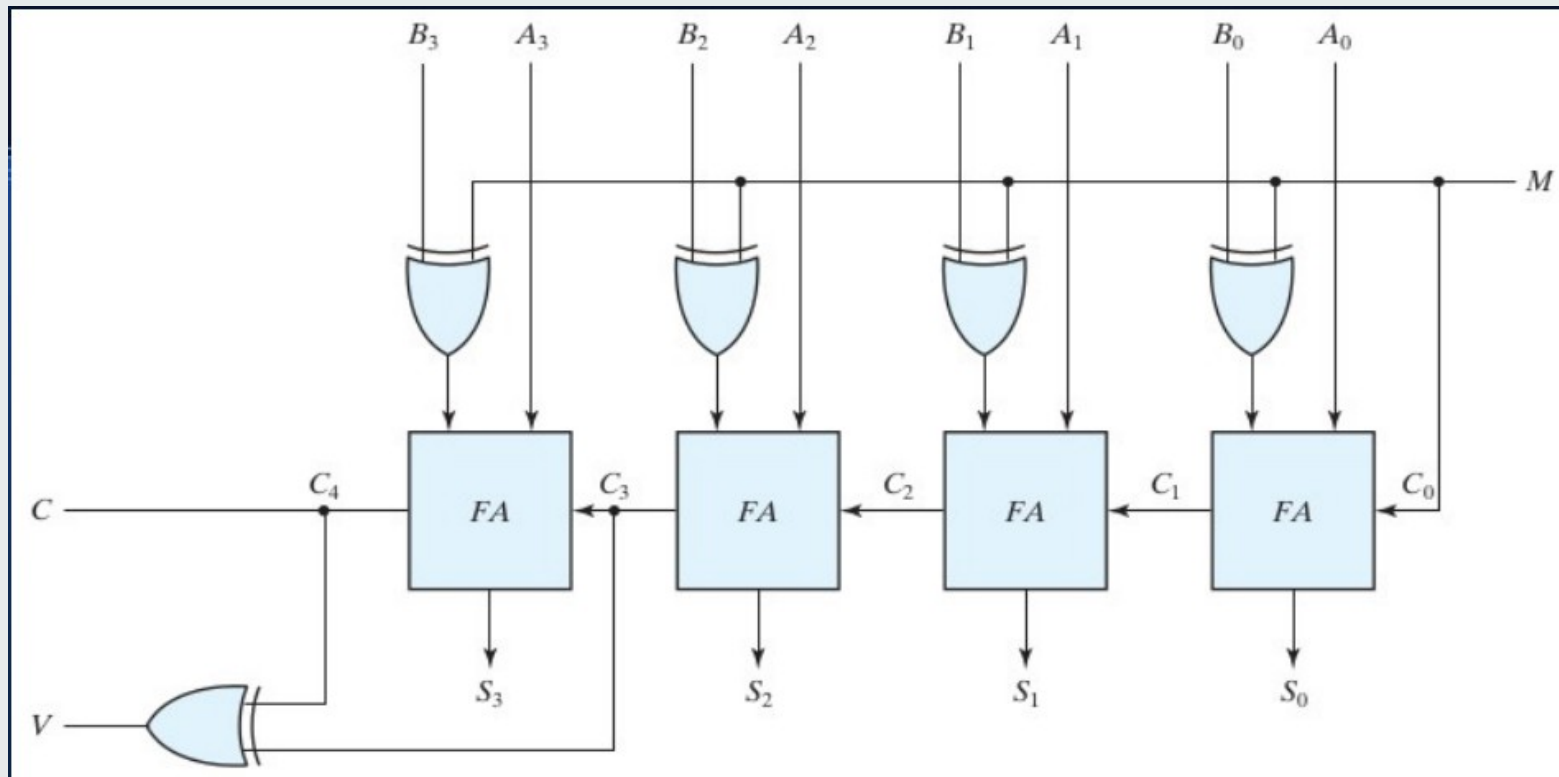

Sign extension

- Sometimes we need to increase the number of bits for representation in different signed integer format
- Sign of the number should be preserved
- Q1: represent signed number **1000** (-8_{10}) with 8 bits
- A1: **1111**1000 (sign extension in red)
- Q2: represent signed number 0111 (7_{10}) with 8 bits
- A2: **0000**0111 (sign extension in red)

Logical/Arithmetic right shift

- Shifting a number **left** by p positions is the same as multiplying it by 2^p
- Shifting a **signed** number **right** by p positions is the same as dividing it by 2^p
- **Sign must be preserved: arithmetic right shift**
- 1000 (-8_{10}) shift right by 2 (divide by 4)
 - Logical right shift **00**10 (2_{10}): **wrong!**
 - Arithmetic right shift **11**10 (-2_{10}): **correct!**

Signed multiplication: fundamentals

- $A = a_3 a_2 a_1 a_0$, $B = b_3 b_2 b_1 b_0$

- In decimal notation

$$B = -b_3 \cdot 2^3 + b_2 \cdot 2^2 + b_1 \cdot 2^1 + b_0 \cdot 2^0$$

$$A \cdot B = A * [-b_3 \cdot 2^3 + b_2 \cdot 2^2 + b_1 \cdot 2^1 + b_0 \cdot 2^0]$$

- Algorithm:

- Add least significant partial products, subtract most significant partial product

Signed multiplication: circuit

