 


Computer Electronics

Lecture 8: Adder Circuits – Part 2; Amdhal's Law




Amdahl's Law

- One the most important computer architecture laws
- Establish the limits of Acceleration
- A program takes T seconds to execute; a part of the program takes P seconds to execute; if P is accelerated K times than the total Speed-Up SU is given by

$$SU = \frac{T \text{ before acceleration of } P}{T' \text{ after acceleration of } P}$$

$$SU = \frac{T}{T - P + \frac{P}{K}}$$

 

Amdahl's Law Implications


- If P is small do not bother to accelerate it
- Many times, accelerating a task 10 times is as good as accelerating the same task 100000000 times!

$$SU = \frac{T \text{ before acceleration of } P}{T \text{ after acceleration of } P}$$

$$SU = \frac{T}{(T - P) + \frac{P}{K}}$$

Ripple Carry Adder problem: how long will it take for the carry to ripple?

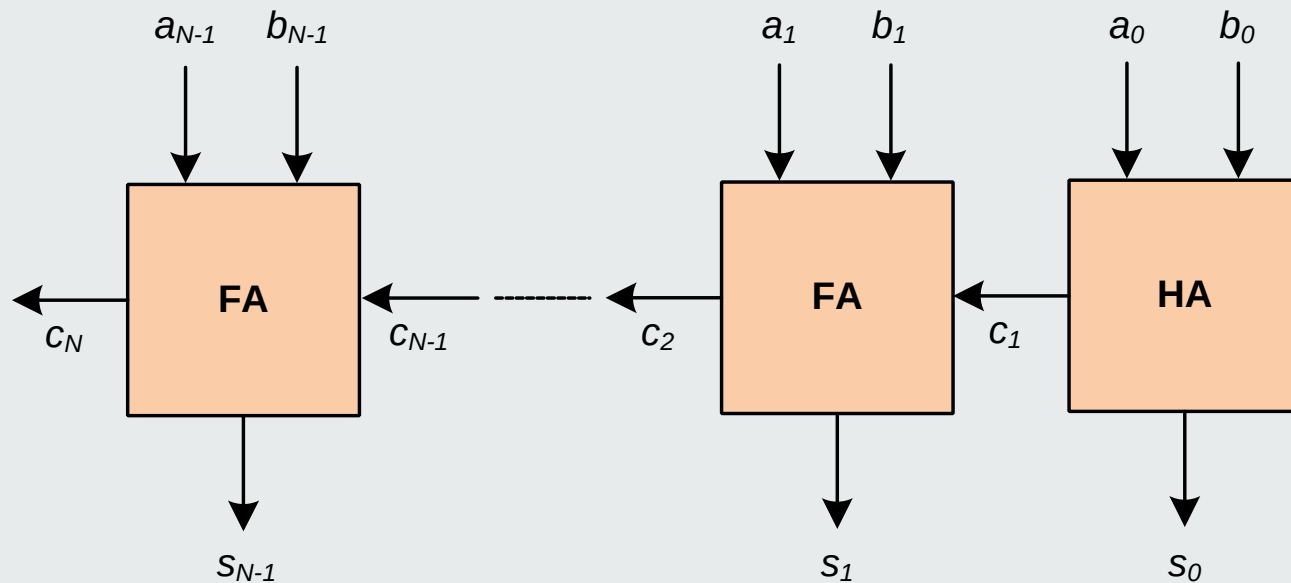- Answer: it will take the time to traverse all single bit adder blocks.... !




The Carry Look-ahead Adder (CLA)


- Speeds up carry computation by using a tree structure instead of a linear structure
- Linear structure length: N
- Tree structure height: $\log(N)$
- Think of $N=1000$: a binary tree height is only 10 – dramatic speedup!!

Carry prediction from inputs


Death

 

Propagation

 

Generation

 

Mathematically

$$g_i = a_i \cdot b_i$$

$$p_i = a_i \oplus b_i$$

$$c_{i+1} = g_i + p_i \cdot c_i$$



Carry recursive computation

$$\begin{aligned}c_{i+1} &= g_i + p_i \cdot c_i \\&= g_i + p_i \cdot (g_{i-1} + p_{i-1} \cdot c_{i-1}) \\&= g_i + p_i \cdot g_{i-1} + p_i \cdot p_{i-1} \cdot (g_{i-2} + p_{i-2} \cdot c_{i-2}) \\&\dots \\&= g_i + p_i \cdot g_{i-1} + p_i \cdot p_{i-1} \cdot g_{i-2} + p_i \cdot p_{i-1} \cdot p_{i-2} \cdot g_{i-3} + \dots + p_i \cdot p_{i-1} \cdots p_1 \cdot p_0 \cdot c_0\end{aligned}$$




- Can use a 2-level SUM OF PRODUCTS circuit
- Multi-input OR and AND gates
- Implement as 2-input gate trees!
- **CARRY AS TREE FUNCTION OF ALL INPUTS!**

Block Carry Look-ahead Adder


Combine CLA and RCA

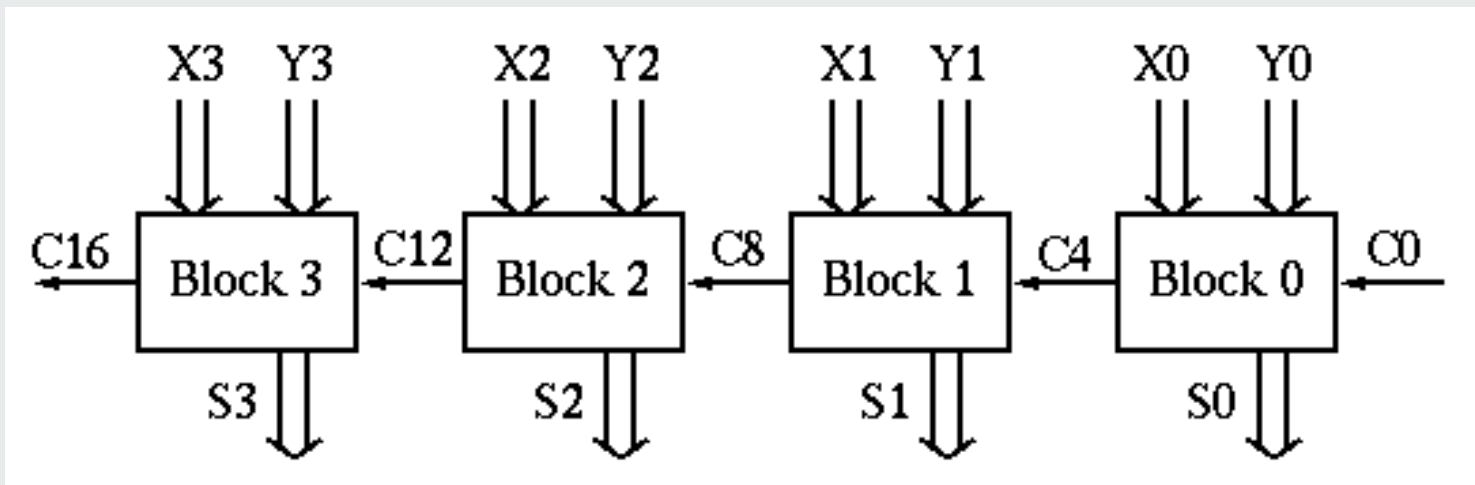 


Using multiple levels

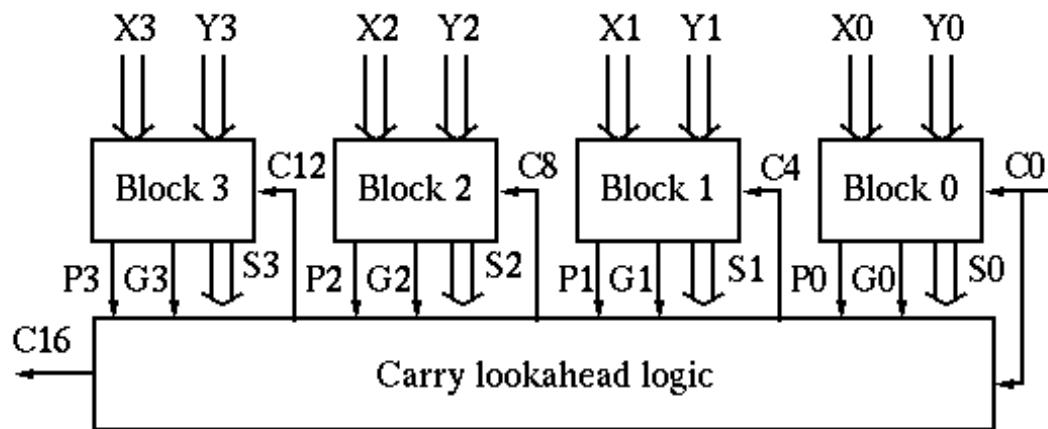  


Tree Carry Look-Ahead Adder

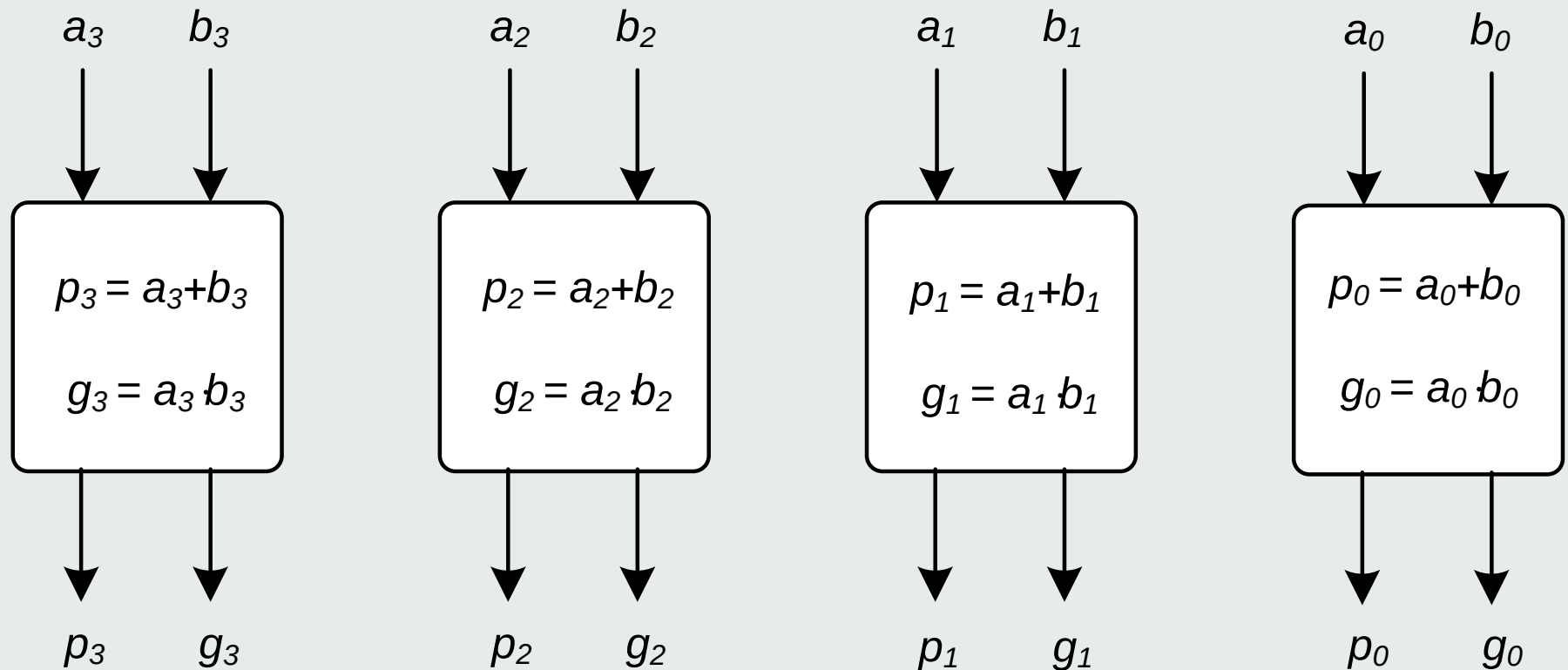

Tree Carry Look-Ahead Adder

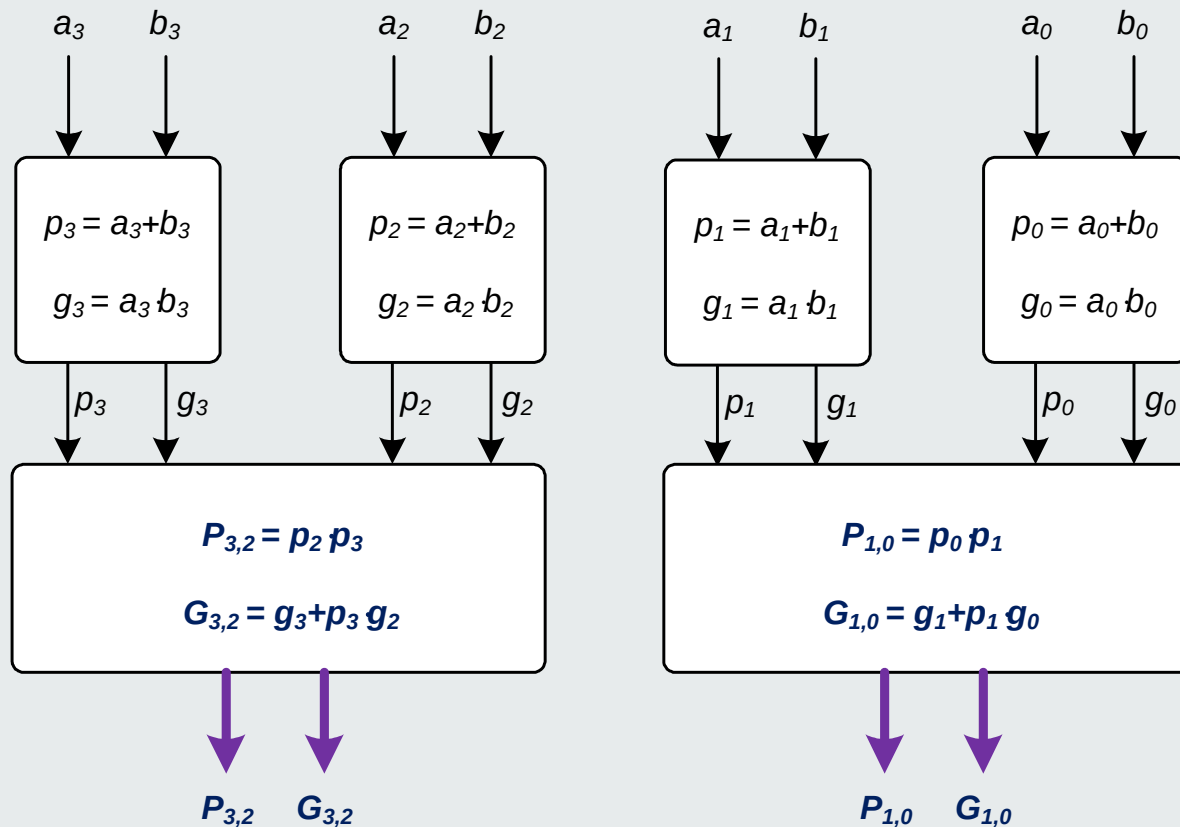


Carry Look-Ahead Tree

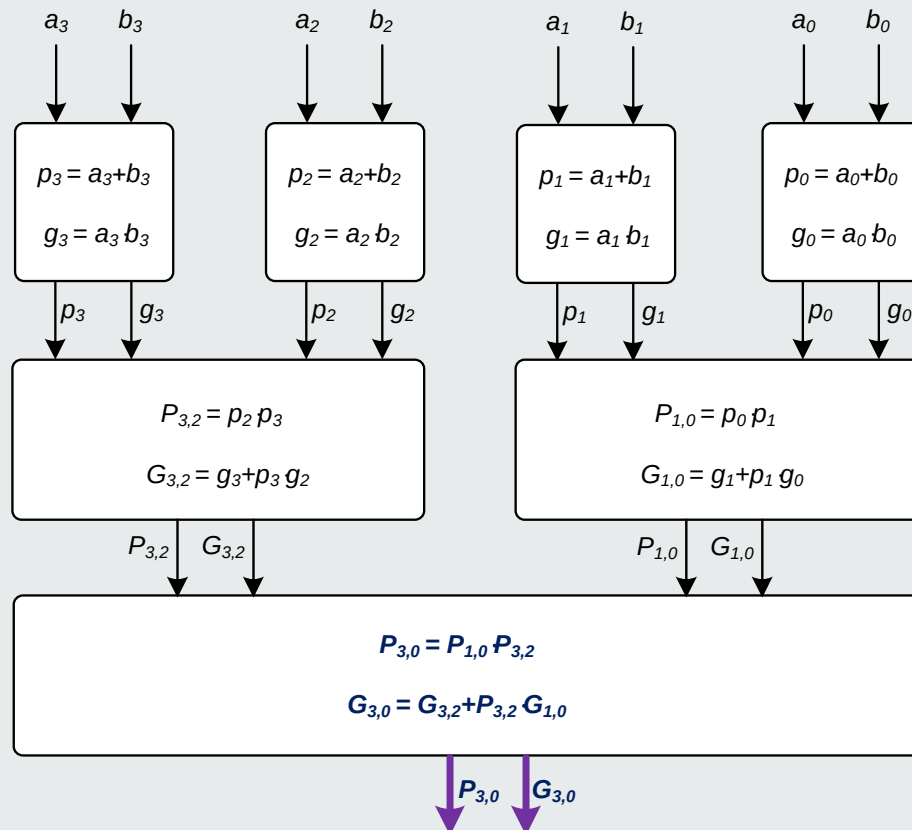

Carry out of a block

$$C_{k+1} = G_{k,i} + P_{k,i} \cdot C_i$$

4-bit CLA

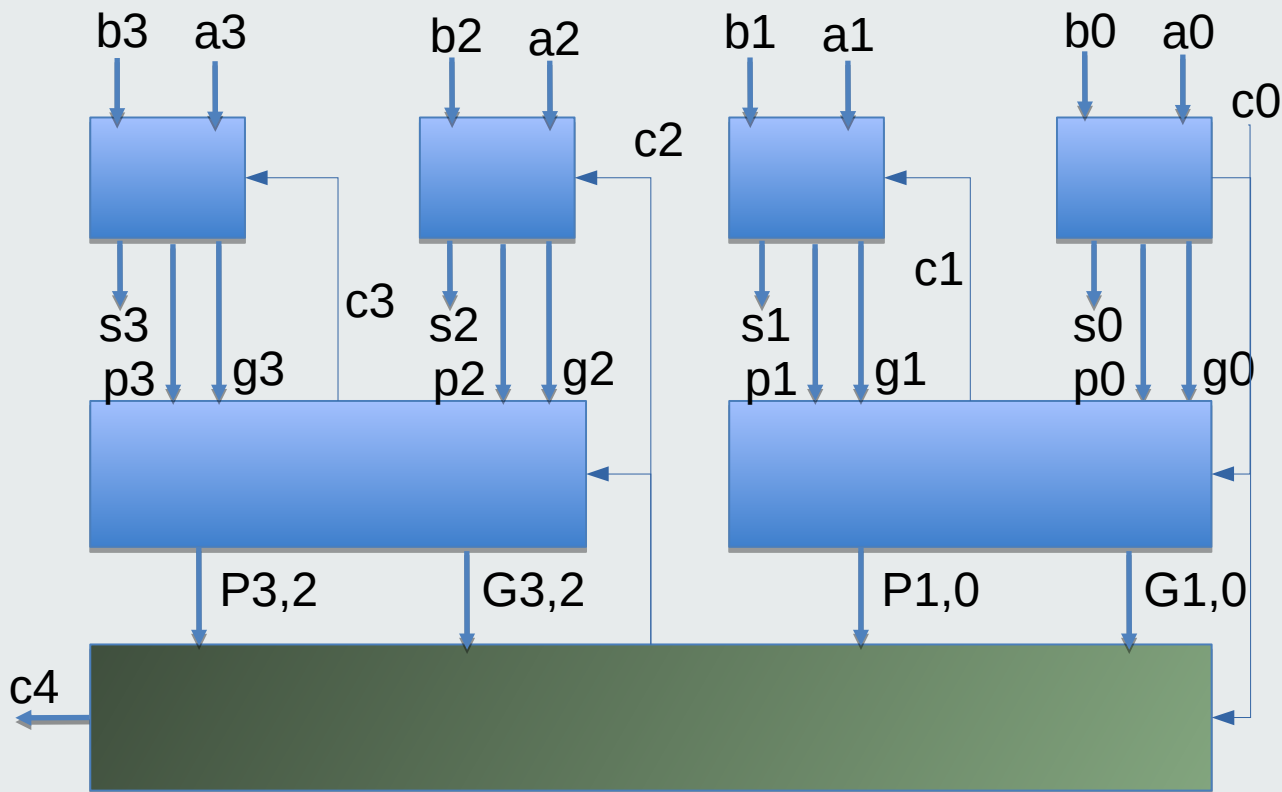

$$\begin{aligned} s_0 &= a_0 \text{ XOR } b_0 \text{ XOR } c_0 \\ p_0 &= a_0 \text{ XOR } b_0 \\ g_0 &= a_0 * b_0 \end{aligned}$$


$$\begin{aligned} P_{1,0} &= p_1 * p_0 \\ G_{1,0} &= g_1 + p_1 * g_0 \\ c_1 &= g_0 + p_0 * c_0 \end{aligned}$$

$$\begin{aligned} P_{3,0} &= P_{3,2} * P_{1,0} \\ G_{3,0} &= G_{3,2} + P_{3,2} * G_{1,0} \\ c_2 &= G_{1,0} + P_{1,0} * c_0 \end{aligned}$$

$$c_4 = G_{3,0} + P_{3,0} * c_0$$

Critical Path Length = $2 * \log(N) * (\text{Node delay})$

Worksheet 8: design this Verilog

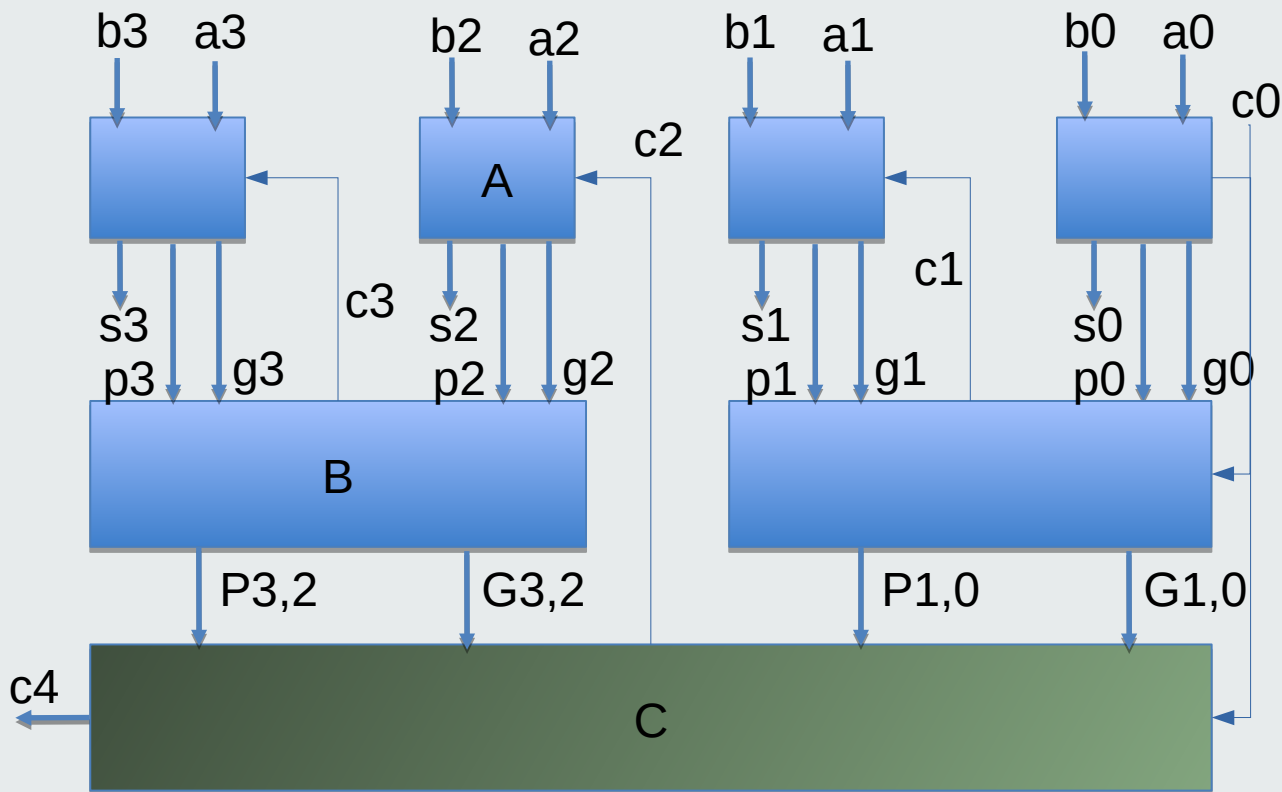

$$s0 = a0 \text{ XOR } b0 \text{ XOR } c0$$

$$p0 = a0 \text{ XOR } b0$$

$$g0 = a0 * b0$$

$$P1,0 = p1 * p0$$

$$G1,0 = g1 + p1 * g0$$

$$c1 = g0 + p0 * c0$$

$$P3,0 = P3,2 * P1,0$$

$$G3,0 = G3,2 + P3,2 * G1,0$$

$$c2 = G1,0 + P1,0 * c0$$

$$c4 = G3,0 + P3,0 * c0$$

Critical Path Length = $2 * \log(N) * (\text{Node delay})$