 


Computer Electronics


Lecture 7: Digital Circuits and Verilog II

The FLIP-FLOP!



- Only D type is studied
- Verilog description is directly mapped to a library component
- Set (S) and Reset (R) are optional
- It is rare that S and R are simultaneously supported: no library component
- Responds to the rising (positive) edge of the clock (CLK)
- Responds to the falling (negative) edge of the clock if an inverter is placed at the CLK input (DANGER ZONE!)
- The optional Enable signal (EN) determines whether the flip-flop will respond or not to the clock edge

Recap: just learn 2 things!

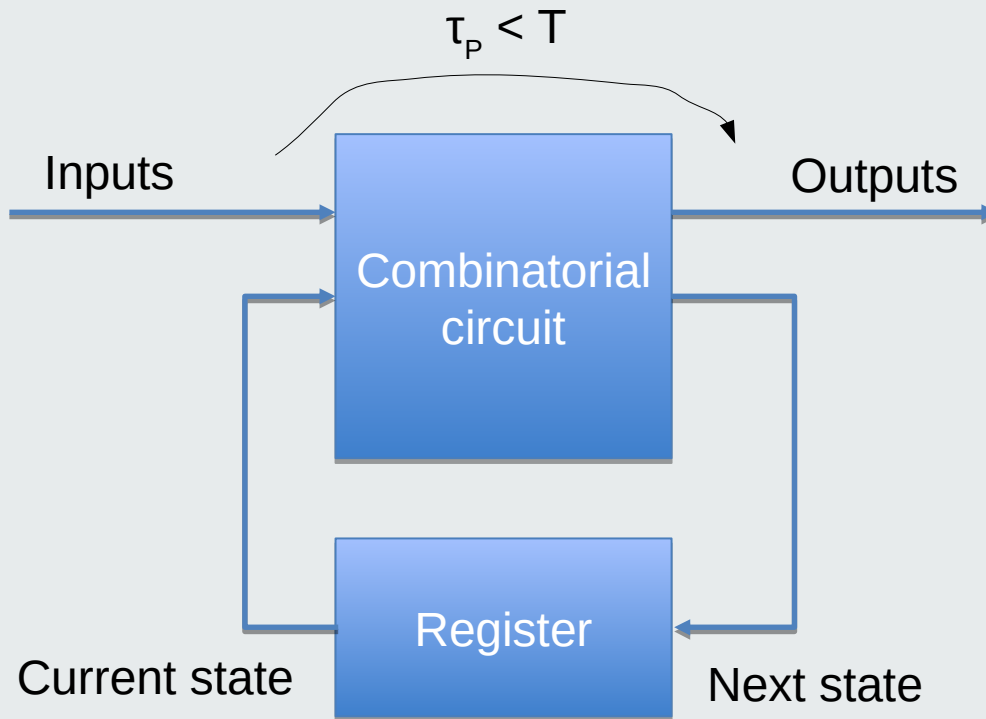

- If any digital circuit is just this then you just need to learn to describe:
 - combinatorial circuits
 - registers
- Not bad, is that?

Signal wires

- Verilog describes circuits
- Circuits are blocks connected by wires that carry digital signals (0 or 1)
- So we need to declare and use wires
- Verilog describes two types of wires: *wire* and *reg*
- And the mess begins:
 - A *wire* is a wire but it cannot be used in all situations
 - A *reg* is a wire (not a register as the name suggests) but it cannot be used in all situations
- What a start!!!

iob-lib: making digital hardware design easy

- <https://github.com/IObundle/iob-lib>
- The **iob-lib** repo contains
 - Useful Verilog **macros** to avoid writing the same Verilog description over and over again
 - Useful **components** (modules) to avoid writing the same Verilog description over and over again
- Enjoy!

IOb-lib: input and output ports

- To declare a module:

```
module my_module  
(  
  `INPUT(X,8), //declare 8-bit input  
  `INPUT(Y,8),  
  `OUTPUT(Z,16) //declare 16-bit output  
  `INOUT(F,32) //declare 32-bit bidirectional port  
);  
  <body of module>  
endmodule
```

IOb-lib: instantiate components


- To instantiate a component is same as in Verilog:

```
module my_system
(
  `OUTPUT( C),
  //interface signals
);
  <body verilog code: preamble>

  my_module comp0 //component instance
  (
    .X(A), //component port
    .Y(B),
    .Z ( C), //is output
    .F (D)
  )

  <body verilog code: trailer>
endmodule
```

my_system

 

IOb-lib: signals

- To declare a signal:
``SIGNAL(my_wonder_signal, 10)`
- With normal Verilog it would be
- `wire [9:0] my_wonder_signal;`
- **`reg [9:0] my_wonder_signal;`**
- `wire [0:9] my_wonder_signal;`
- Etc...

IOb-lib: signed signals

- To declare a signed signal:
`SIGNAL_SIGNED(my_wonder_signal, 10)
- With normal Verilog it would be
- wire signed [9:0] my_wonder_signal;
- **reg signed [9:0] my_wonder_signal;**
- wire signed [0:9] my_wonder_signal;
- Etc...

IOb-lib: special signals that can be used as outputs

- To get around the complexities of Verilog a special signal type is created in iob-lib:

``SIGNAL_OUT(my_special_signal, 10)`

- Used to connect to component outputs
- Connecting a ``SIGNAL` to a component output is an ERROR
- Cannot be used as the result of computations (to be explained)
- Using ``SIGNAL_OUT` as the result of a computation is an ERROR
- With normal Verilog it would be
 - You don't want to know!!

IOb-lib: using `SIGNAL_OUT


```

module my_system
(
  //interface signals
  //`OUTPUT(C,16) is also an alternative
);
  <body verilog code: preamble>
  `SIGNAL_OUT(C,16)    //`SIGNAL(C,16) is an ERROR)

  my_module comp0 //component instance
  (
    .X(A), //component port
    .Y(B),
    .Z(C)
  )

  <body verilog code: trailer>
endmodule
  
```

my_system

 


IOb-lib: flip-flops

- Flip-flop: stores 1 bit

```
`SIGNAL(D,1)  //declare input signal D  
`SIGNAL(Q,1)  //declare output signal Q  
`REG(clk, Q, D) //instantiate one flip-flop
```

IOb-lib: registers!

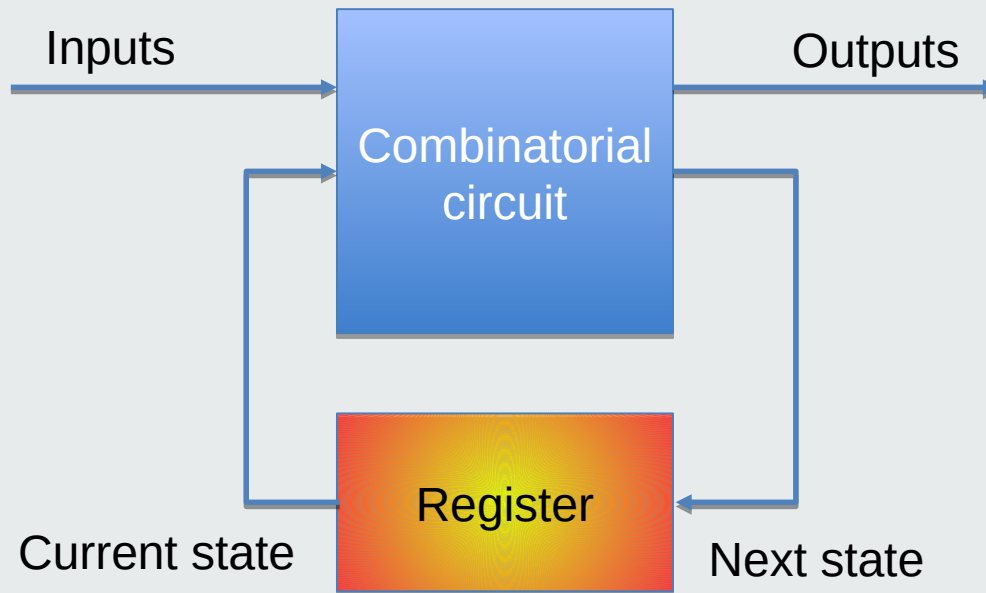


IOb-lib: registers

- Register: stores W bits

```
`SIGNAL(D,10) //declare input signal vector D  
`SIGNAL(Q,10) //declare output signal vector Q  
`REG(clk, Q, D) //instantiate register or flip-flop  
//array
```

IOb-lib: combinatorial circuits

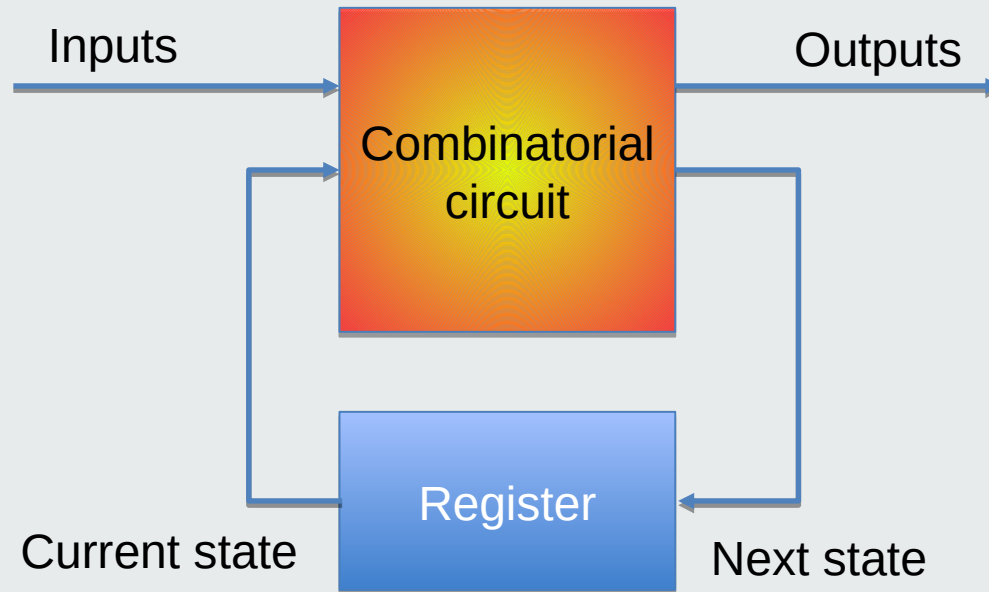

IOb-lib: combinatorial blocks

```
module my_system
(
  //interface signals
);
...
`SIGNAL(z,10);
`SIGNAL(y,10);
`COMB begin
  //insert C-like expressions here: examples
  z = s? X: Y;
  y = a*(b+c);
  //IMPORTANT: z and y MUST be of type `SIGNAL: type `OUTPUT or `SIGNAL_OUT are ERROR!!!
end
...
endmodule
```


IOb-lib: combinatorial block result to output problem

- So how to assign an output to the output of a combinatorial circuit?
- Answer: use signal to output conversion function

```
module my_system
```

```
(
```

```
`OUTPUT(Z, 10);
```

```
//other interface signals
```

```
);
```

```
...
```

```
`SIGNAL(z,10)
```

```
`COMB begin
```

```
...
```

```
z = s? X: Y;
```

```
...
```

```
end
```

```
`SIGNAL2OUT(Z,z)
```

```
...
```

```
endmodule
```

IOb-lib: order of statements

```
module my_system
(
  //interface signals
);
...
`SIGNAL(z,10); //important to keep here
`SIGNAL(y,10);

`SIGNAL2OUT(Z,z) //not important to keep here
`COMB begin
  //insert C-like expressions here: examples
  z = s? X: Y;
  y = a*(b+c);
  //IMPORTANT: z and y MUST be of type `SIGNAL: type `OUTPUT or `SIGNAL_OUT are ERROR!!!
end
  //`SIGNAL2OUT(Z,z) //could be here...
endmodule
```

- In Verilog the order of statements is **irrelevant** since we are describing things, not procedures!
- Signal declarations must precede their use
- Inside a combinatorial block order is important because it is ***described procedurally***
- Only the result of the combinatorial block matters and this may be affected by order