

# Computer Electronics

## Lecture 15: Adder Circuits – Part 1

# Typical ALU operations


- Arithmetic: Addition, subtraction
- Logical: NOT, AND, OR, XOR, ...
- Less common (normally performed by dedicated FUs):
  - Bit shifting: left, right (logical or arithmetic)
  - Multiplication
  - Division

# Why only simple operations?

- Complex operations require more hardware whose cost must be justified
- Complex functions can be decomposed as a time sequence of simple operations
- Certain complex functions can be added as needed:
  - Dedicated IP cores integrated in the same chip
  - Dedicated chips integrated in the same board
 
# The origin of the ALU

- John von Neumann proposed it
- EDVAC computer, 1945




# Integer number representation

- Binary: easy to implement and robust to noise
- Resolution: number of bits,  $N$
- Unsigned numbers:  $0, 1, 2, \dots, 2^N-1$
- Signed numbers:  $-2^{N-1}, -2^{N-1}+1, \dots, -1, 0, +1, \dots, 2^{N-1}-1$
- Signed numbers: 2's complement representation normally used
 
# How to compute the 2's complement

- Method 0: (software)
  - $\text{complement2two}(x) = 2^N - x$
- Method 1: (hardware)
  - Invert all bits
  - Add 1
- Method 2: (hand, hardware?)
  - Scan number from right to left
  - Up to the first 1 inclusively: leave unchanged
  - Invert all remaining bits



# Adder circuits

- Addition is the most basic arithmetic operation
- Basis for more complex operations, like multiplication, division, etc
- Different possible implementations
  - Simple implementation: small and *cool* (low power), high combinational delay
  - Elaborate implementation: big and *hot* (high power), low combinational delay
- Technology used influences architecture choice
  - FPGA use the simplest, for example

## Unsigned addition

$$1010 + 0011 = 10_{10} + 3_{10}$$

Overflow happens if  
result < some operand

$$1010 \rightarrow 10$$

$$\underline{+0011} \rightarrow 3$$

$$1101 \rightarrow 13$$

$$0010 \rightarrow \text{Carry}$$

$$1010 \rightarrow 10$$

$$\underline{+1010} \rightarrow 10$$

$$0100 \rightarrow 4 (!)$$

$$1010 \rightarrow \text{Carry}$$




# Visualizing and computing unsigned addition and overflow

$$10 + 12 = 6!$$

$$\begin{array}{r} 1010 \\ +1100 \\ \hline 0110 \end{array}$$

**1**000 → carry on MSB is overflow

 

## Signed addition

$$-3 - 2 = -5$$

$$\begin{array}{r} 1101 \\ +1110 \\ \hline \end{array}$$

$$1011$$

$$\mathbf{1100} \rightarrow \text{carry}$$

Overflow happens if addition of 2 positives (negatives) is a negative (positive)


$$\begin{array}{r} 1010 \rightarrow -6, \text{ negative} \\ +1011 \rightarrow -5, \text{ negative} \\ \hline \end{array}$$

$$\hline$$

$$0111 \rightarrow 7!, \text{ positive!}$$

$$\mathbf{1010} \rightarrow \text{carry}$$
 
# Visualizing and computing signed addition and overflow



How to flag signed addition overflow in hardware?

Overflow = (result\_sign XOR a\_sign)  
AND (a\_sign XNOR b\_sign)


Equivalent to  
Overflow = C(n-1) XOR C(n-2)

Can you prove this?

# Unsigned vs. signed addition

- Same adder hardware is used!!
  - Greatest advantage of 2s complement!
  - Unsigned and signed interpreted differently but addition operation is the same
- Overflow detection
  - Unsigned:  $\text{Carry}(n-1)$
  - Signed:  $\text{Carry}(n-1) \text{ XOR } \text{Carry}(n-2)$

# Ripple carry adder

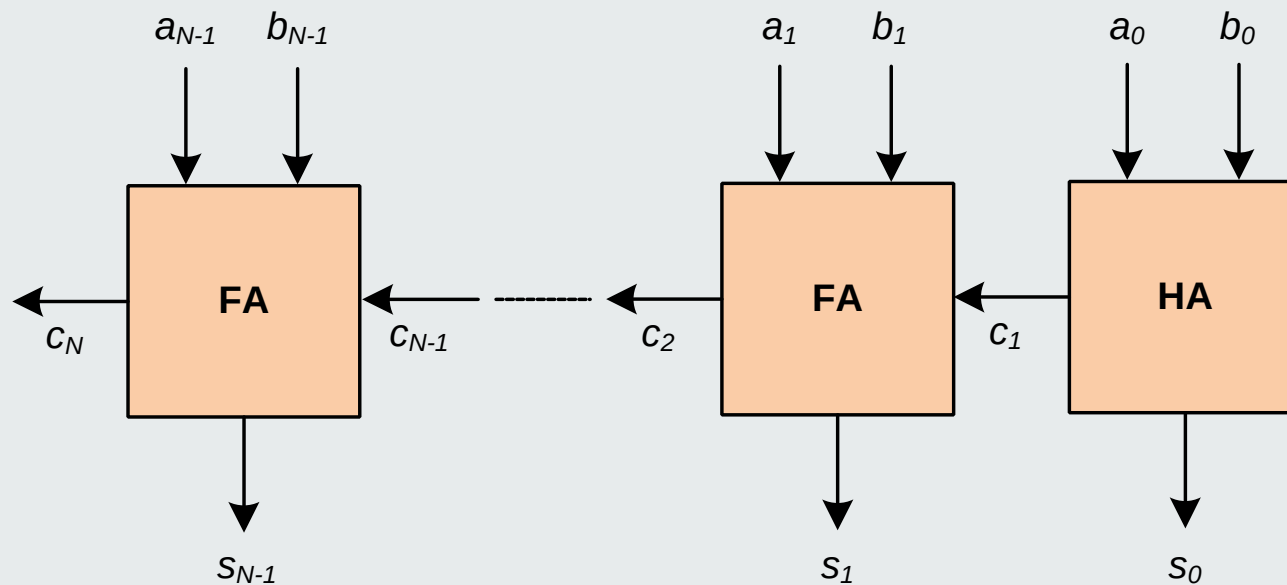

# Half Adder (HA) truth table

- No input carry

$$s_i = a_i \bar{b}_i + \bar{a}_i b_i = a_i \oplus b_i$$


$$c_{i+1} = a_i b_i$$

Inputs		Outputs	
$a_i$	$b_i$	$c_0$	$s_{i+1}$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Half adder logic circuit

$$s_i = a_i \bar{b}_i + \bar{a}_i b_i = a_i \oplus b_i$$

$$c_{i+1} = a_i b_i$$

 

Area: 2 gates  
Delay: 1 gate

# Full Adder truth table

- Input carry

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

$$a_i b_i = g_i \quad \text{Generate}$$


$$a_i + b_i = g_i \quad \text{Propagate}$$

Inputs			Outputs	
$a_i$	$b_i$	$c_i$	$c_0$	$s_{i+1}$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


 
# Full Adder logic circuit

- Area: 6 (2-input) gates
- Propagation delay: 3 gate delays



Carry delays will  
add up when  
blocks chained!

# Full Adder simplification


$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

$$c_{i+1} = a_i b_i + (a_i \oplus b_i + a_i b_i) c_i$$

$$c_{i+1} = a_i b_i (1 + c_i) + (a_i \oplus b_i) c_i$$

$$c_{i+1} = a_i b_i + (a_i \oplus b_i) c_i$$

 
- Area: 5 gates (1 less!)
- Delay: 3 gates (same)




Carry delays  
will add up!

# Ripple carry adder


- Compute area and delay

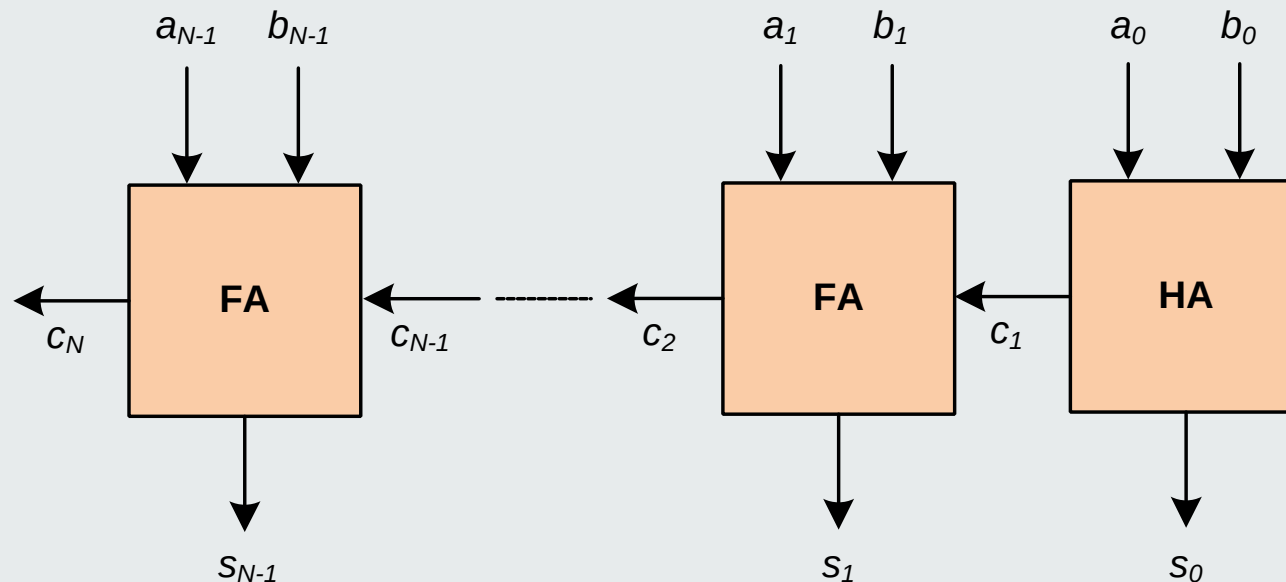

# RCA: compute unsigned overflow

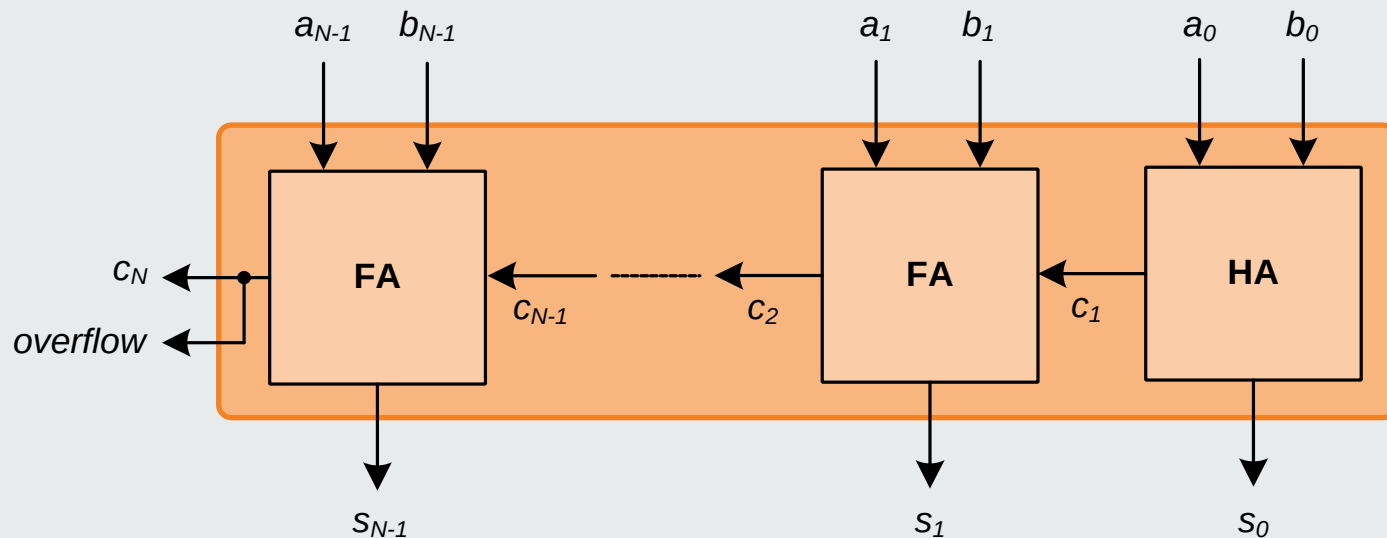


# RCA: compute signed overflow

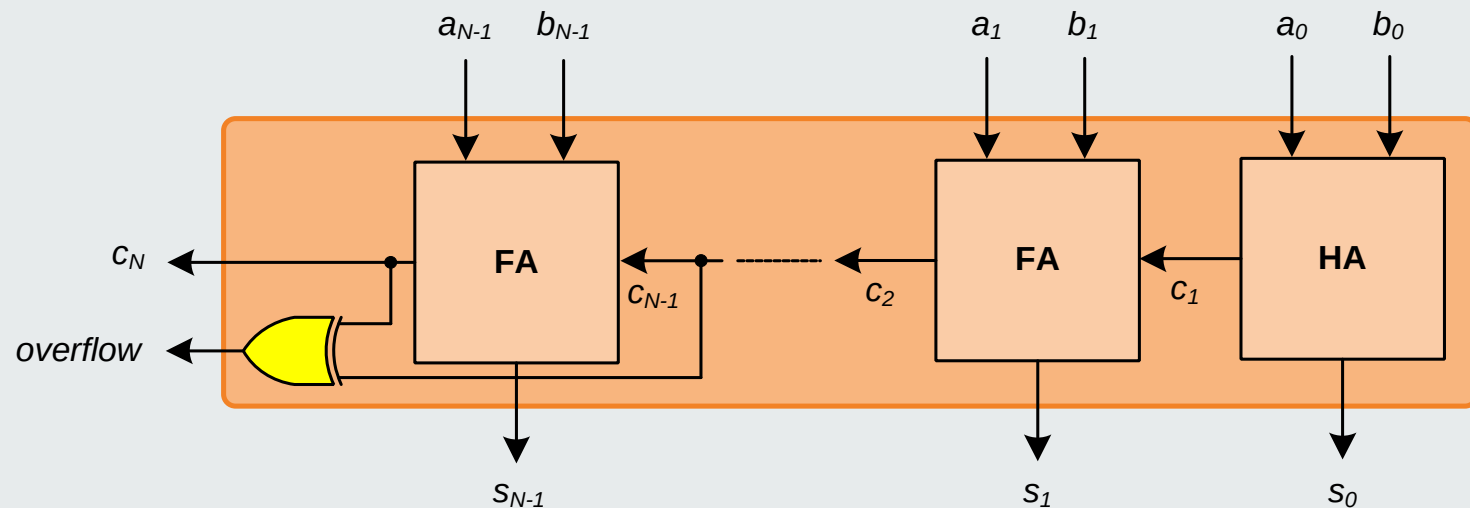

## RCA: advantage and disadvantage

- Advantage: simplest adder circuit, lowest area and power dissipation
- Disadvantage: it is slow
  - Delay is  $O(N)$ , where  $N$  is number of bits
  - Because carry computation is sequential:
    - Wait for  $C(i-1)$  to compute  $C(i)$

# Carry-select adder

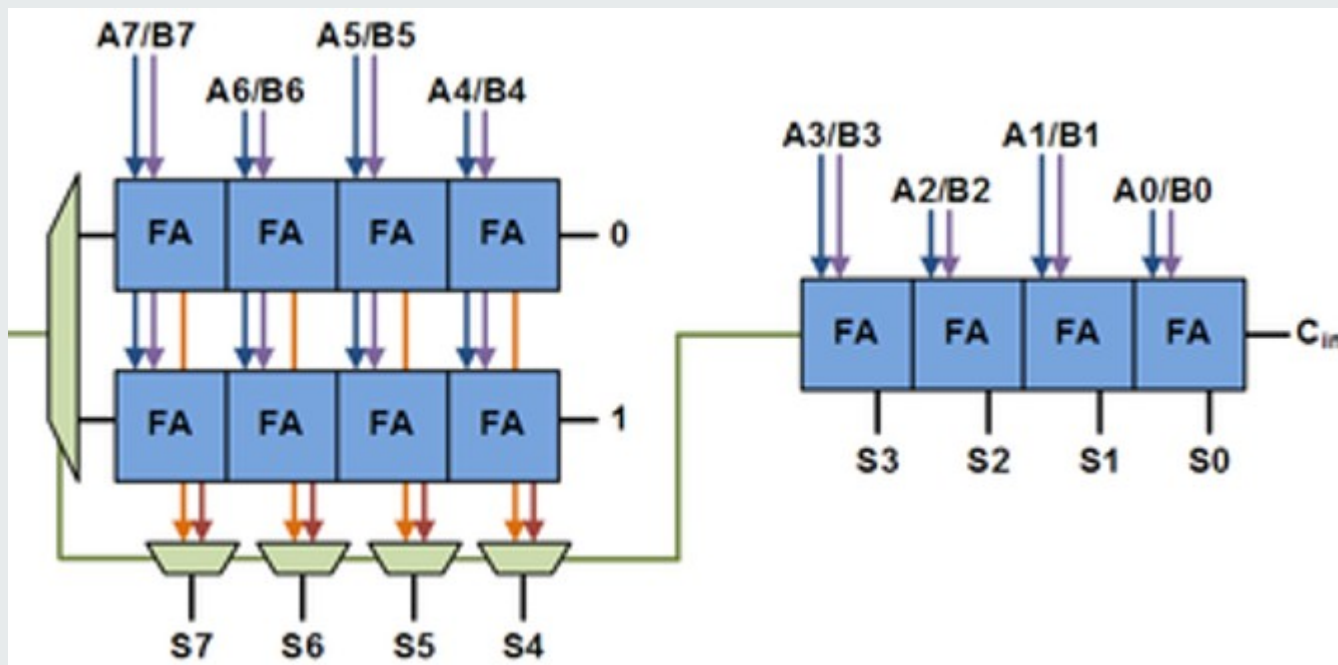

# CSA algorithm summary

- Split N-bit addition into  $N/2$ -bit additions
- Use 1 RCA for lower part (A)
- Use 2 RCAs for higher part (B and C)
  - B assumes carry from lower part is 0
  - C assumes carry from lower part is 1
- Carry A selects the output from either B or C, which had been computed in parallel with A
- CSA delay is half RCA delay + mux delay
- CSA is 100% faster than RCA but 50% larger



Example 32-bit/4-stage:

$$A(\text{CSA})/A(\text{RCA}) = (32+24)\text{FA}/32\text{FA} = 7/4$$

$$\text{Delay}(\text{RCA}) / \text{Delay}(\text{CSA}) = 32\text{FA}/8\text{FA} = 4$$

# K-stage CSA

