

Computer Electronics

Lecture 4: FPGAs

Programmable Hardware

- Designing hardware is challenging, expensive and error prone
- A re-spin of an IC can cost 100s of M\$ in modern nodes (e.g. 22 nm)
- Is there a way to “program circuits” and fix them if there are errors or updates?
- YES: electrically programmable digital circuits!


Field Programmable Gate Array (FPGA)

- Can implement any digital circuit, if it fits in the device
- Useful in prototyping chips
- Traditionally useful in low production volume products
 - 100s of K units and below
 - Beats IC unit costs!
- Clock frequencies well below ICs
- Cheap development cost
 - FPGA tools are cheap, design flow is relatively simple
- Nowadays useful as a general purpose processor, with high production volumes, like GPUs!!


Early FPGA History

- Early 1980
 - Standard IC circuits (microprocessors, bus, I/O controllers, timers, ...) had to be interconnected (serial/parallel, multiplexing, ...)
 - Custom ICs were used for the interconnection logic but had huge cost and long development.
- 1984
 - Xilinx started selling FPGAs
 - Concept invented in 1967 by Wahlstrom
 - No physical layout, no mask making, no IC manufacturing, lower NRE costs and short time to market.


FPGA basic architecture

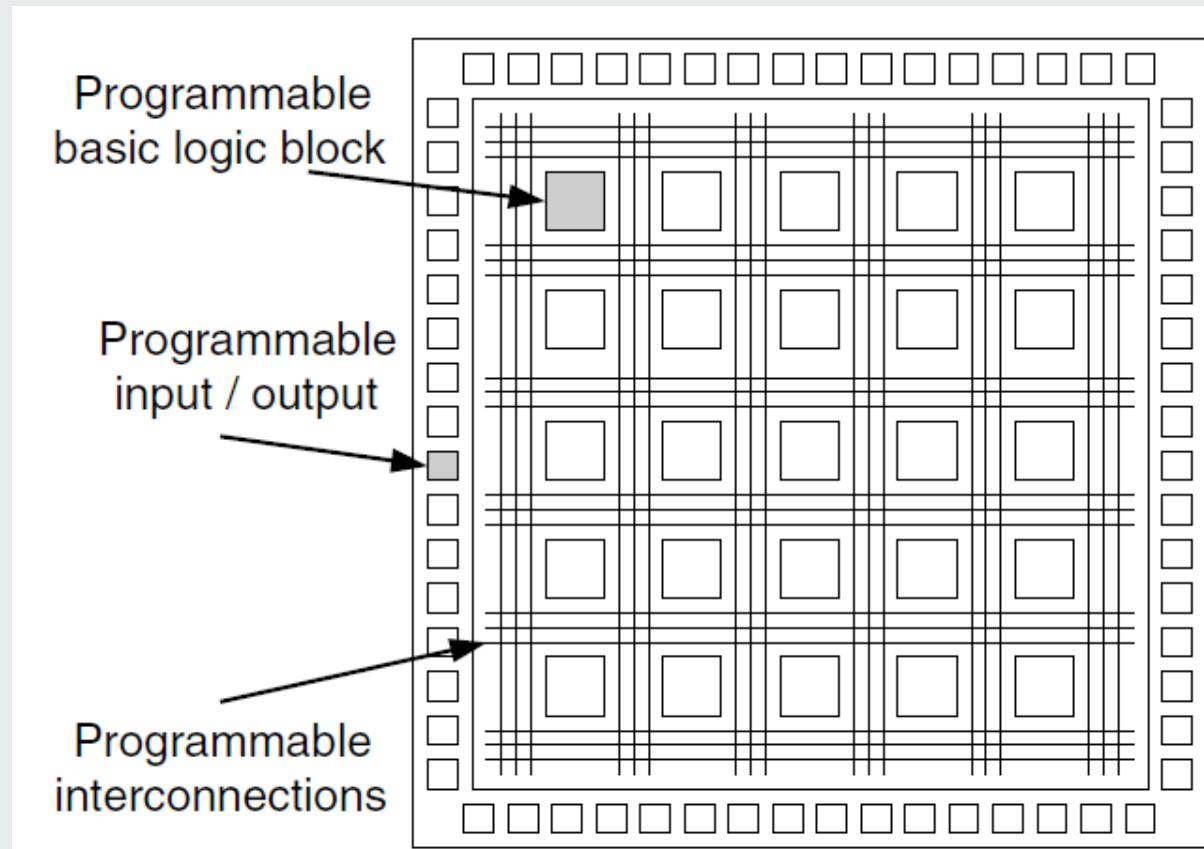


Basic Programmable Logic Block

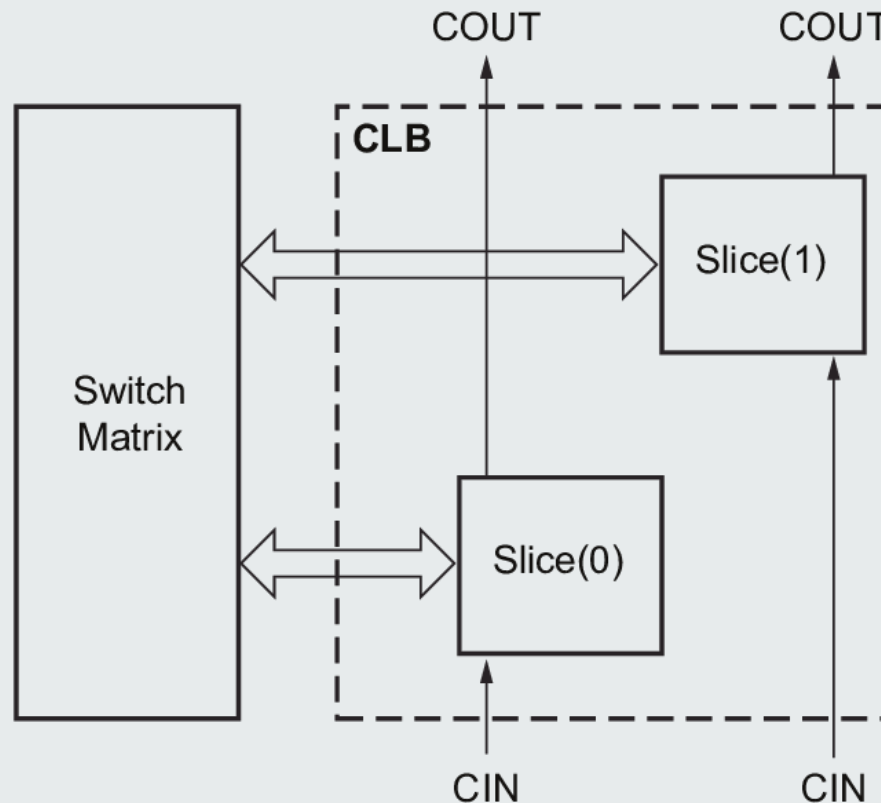

Basic slice

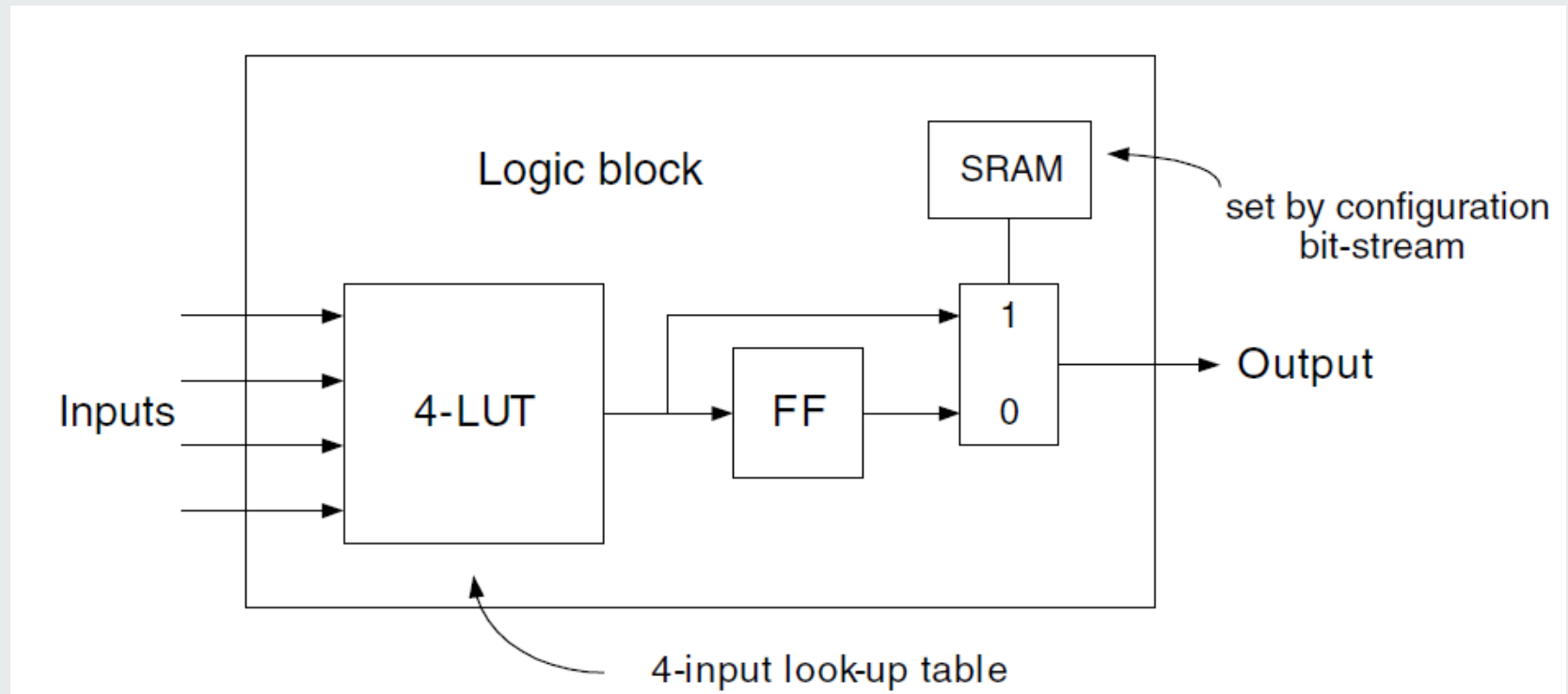


Real slice

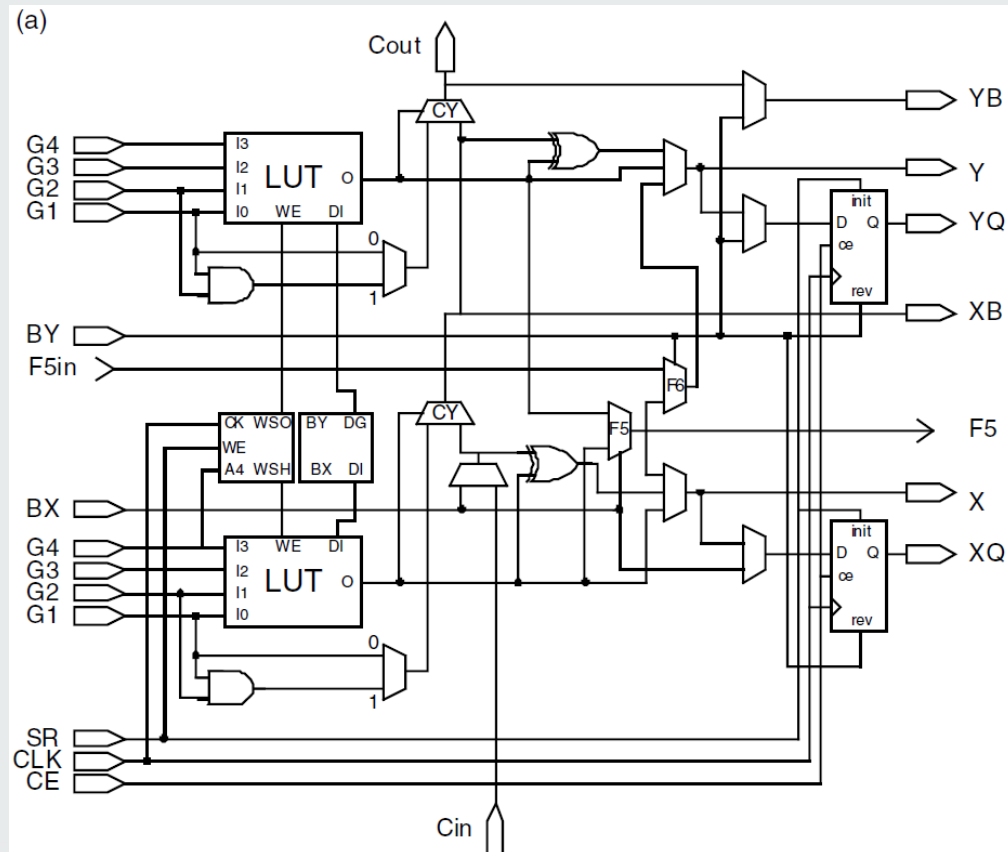


Look-Up Table (LUT)

- Structure: a very small memory
- Implementation: Latch + Multiplexer

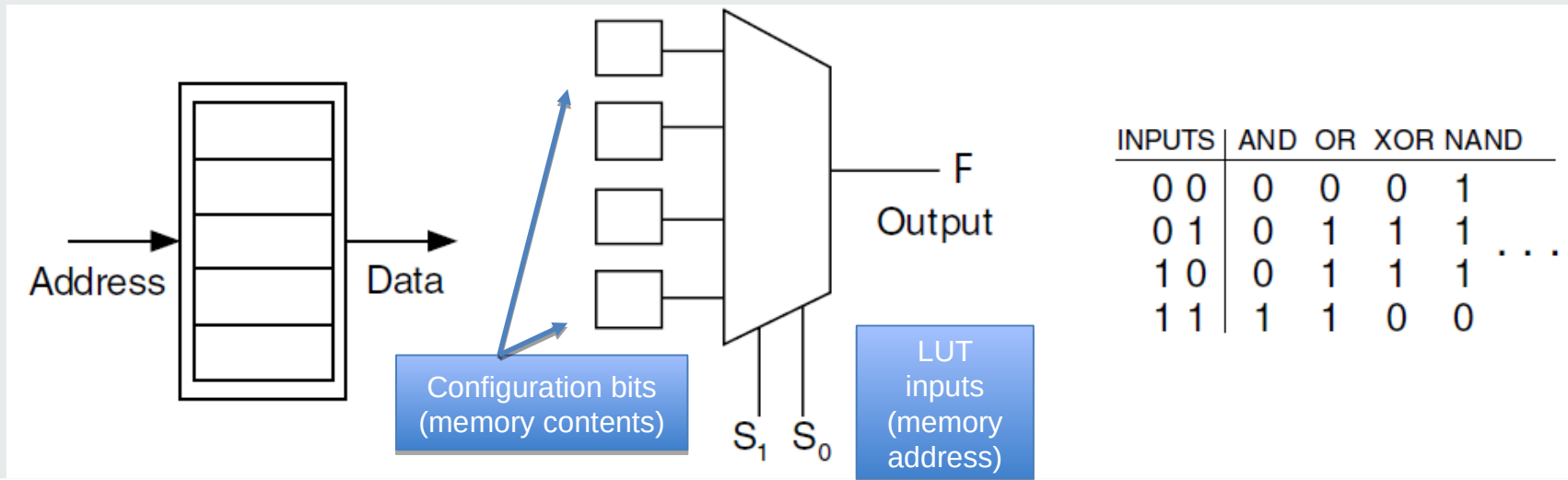


Programmable IO


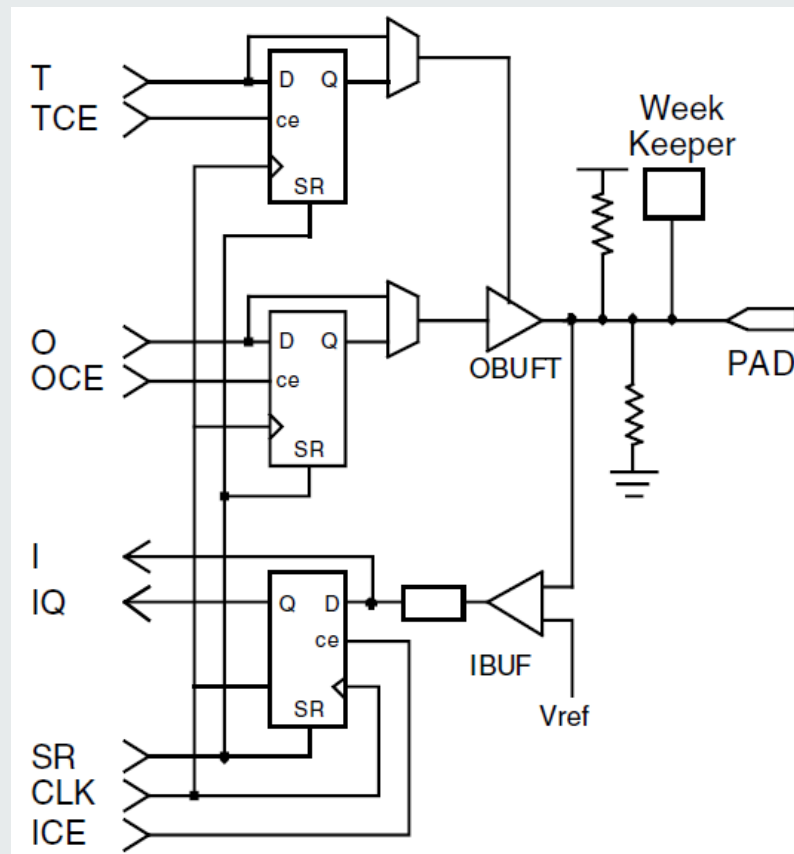


Programmable interconnections

- Local CLB interconnection

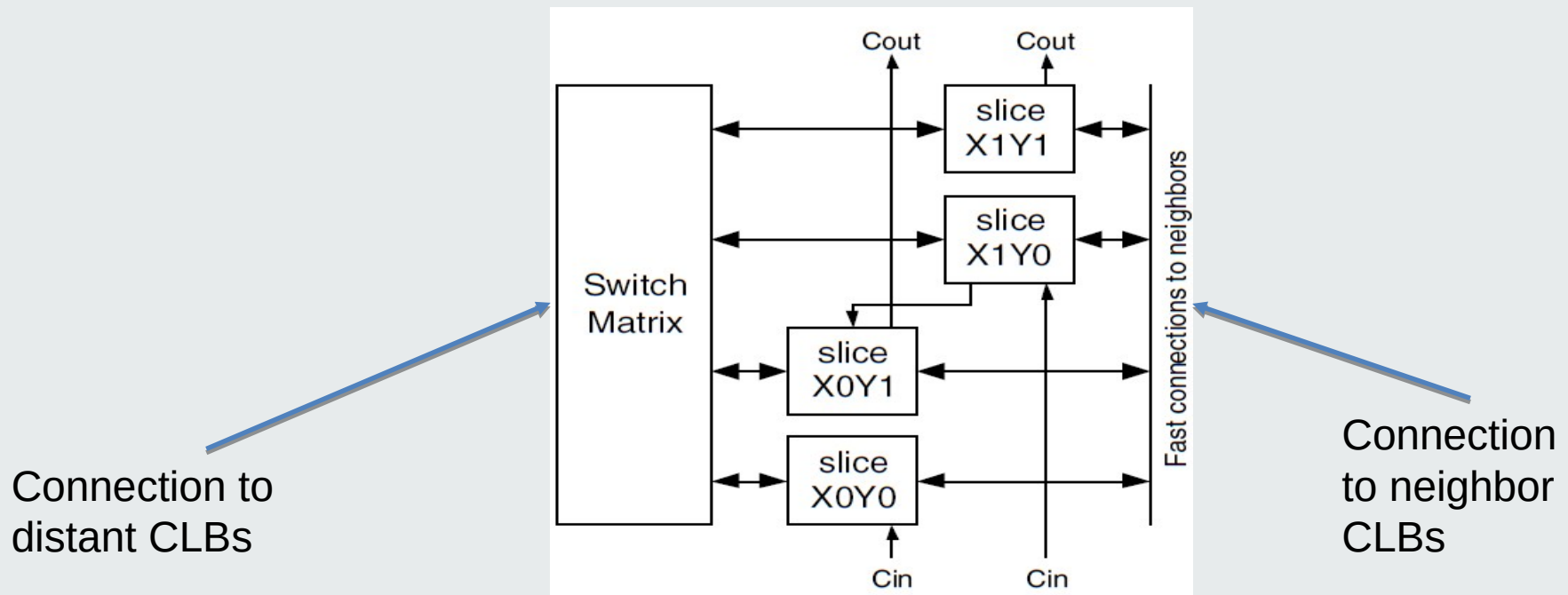

Switch matrices

  


- Configuration bit:
- 0: A not connected to B
 - 1: A connected to B

Interconnect line types

- Long Lines: bidirectional wires that distribute signals across the device. Vertical and horizontal long lines span the full height and width of the device.
- Hex Lines: route signals to every third or sixth block away in all four directions.
- Double Lines: route signals to every first or second block away in all four directions.
- Direct Lines: route signals to neighboring blocks—vertically, horizontally, and diagonally.
- Fast Lines: internal CLB local interconnections from LUT outputs to LUT inputs.

Configuration architecture

- RAM organization

 


Memory and arithmetic

- FPGAs can be programmed to implement registers, register files or larger memories
- The LUTs can be used to implement larger register files or small memories
- FPGAs can be programmed to implement complex arithmetic units such as multipliers
- But, this consumes a lot of LUTs


Heterogenous FPGAs

- Contain embedded RAMs
- Contain embedded DSP blocks
 - Multiply Accumulate units (MACC) and variations
 - Multiply only
 - Add only
 - Multiply an accumulate: mul + add
- Result: better silicon utilization leads to lower price products

FPGA layout

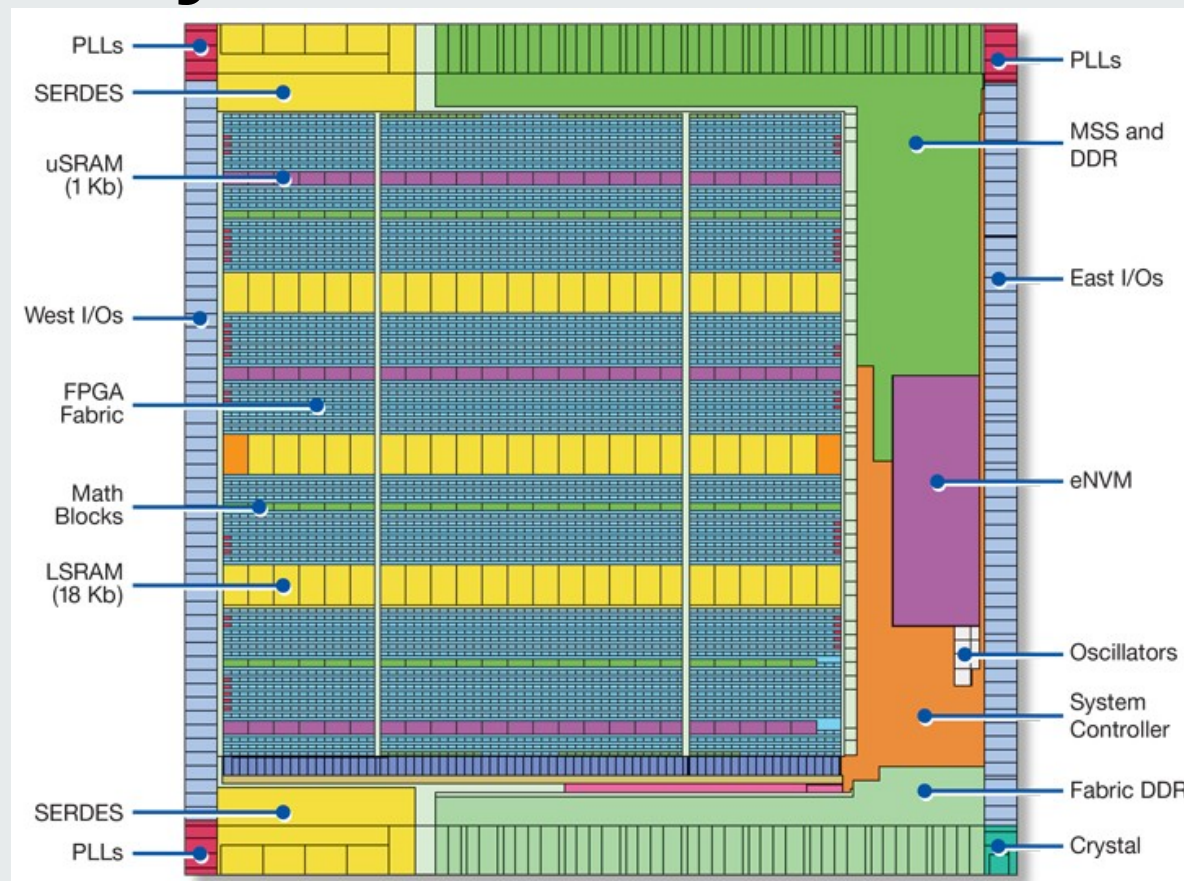


Example FPGA

 


- P0..3: pins, programmable with the following word:
 - Bit 3 – function select bit: input (0) or output (1)
 - Bits 2:1 – select which pin or LUT output
 - Bit 0 – selects FPGA pins (0) or LUT outputs (1);
- L0..3: 2-input (A and B) LUTs, programmable with the following word:
 - Bits 9:6 – function select bits $F(A,B)$
 - Bits 5:3 – input B selection bits;
 - Bits 2:0 – input A selection bits;

Example FPGA

 


FPGA configuration (bitstream)

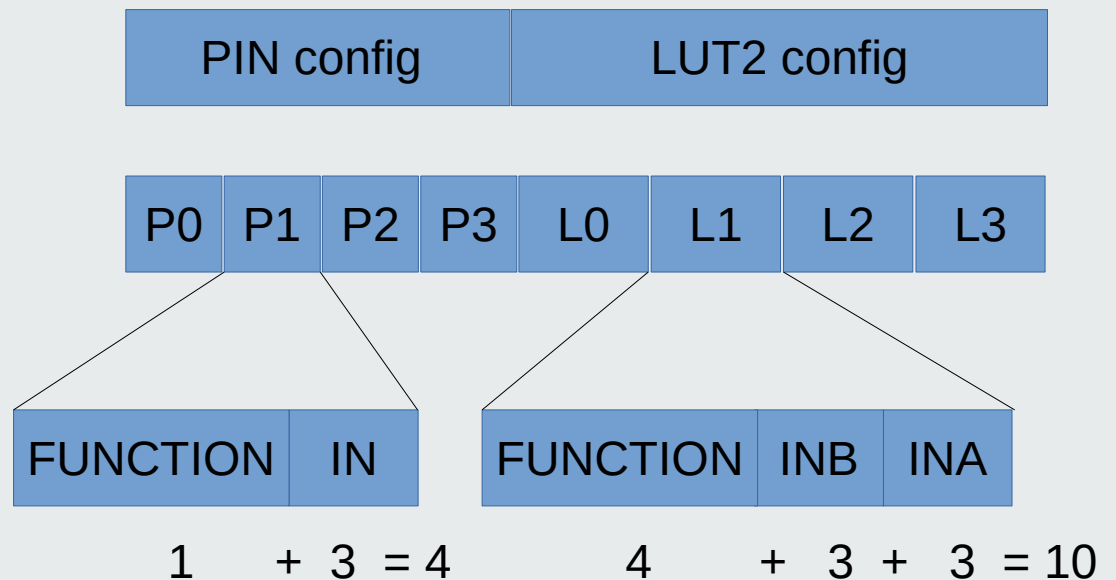

Total configuration bits: $4 \times 4 + 4 \times 10 = 56$ bits

 Example FPGA

Configure logic function $Y = X1 \cdot X2 \cdot X3$



P0..2 are inputs

Config: 0 - - - (0 selects input function, since it is not an output the selection bits are don't care)

P3 is output:

Config: 1 10 1 (1 selects output function, 10 selects L2, 1 selects LUTs)

L0 and L1 are AND2:

L0 config: 1000 01 0 00 0 (1000 selects function AND, 01 0 selects P1 and 00 0 select P0)

L1 config: 1000 10 0 00 1 (1000 selects function AND, 10 0 selects P2 and 00 1 selects L0)

