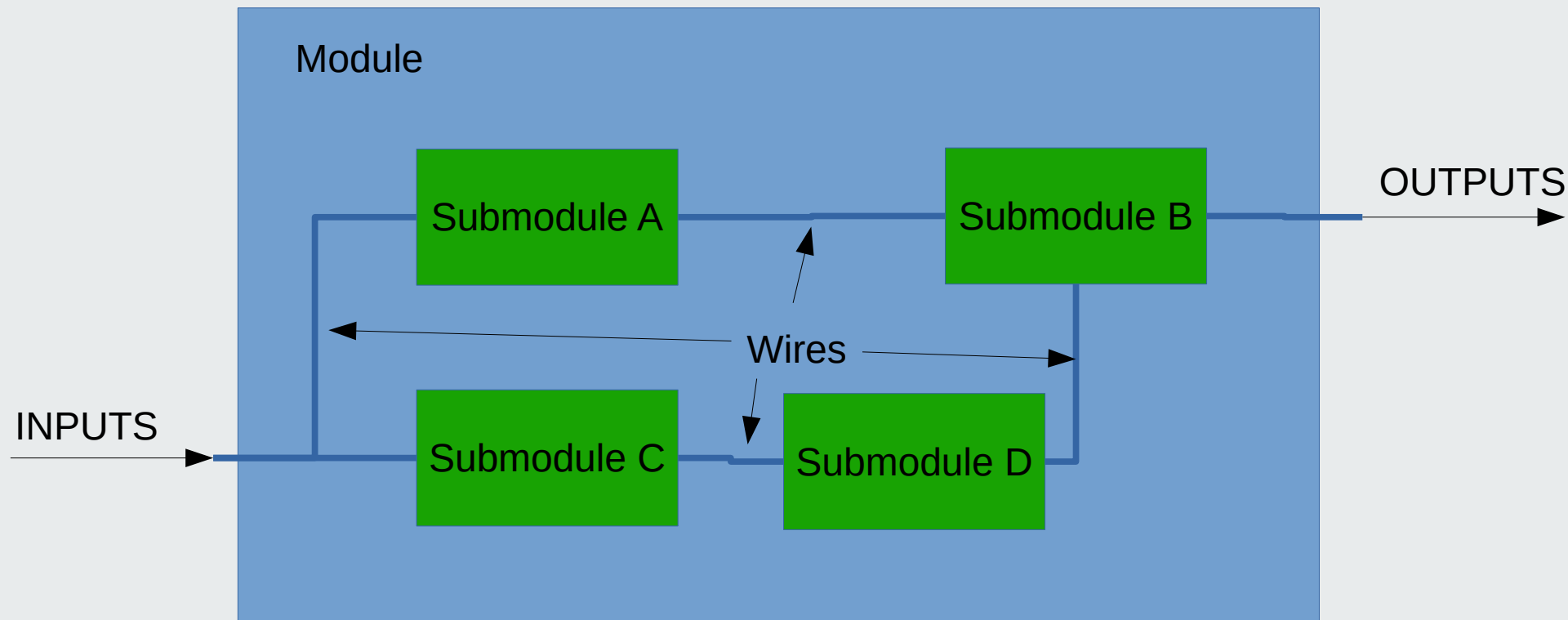


Computer Electronics

Lecture 7: Digital Circuits using Verilog
and IOb-Lib

Modular circuit design




IOb-lib: module interface

```
module my_module (  
    `INPUT(X, 8), //declare 8-bit input  
    `INPUT(Y, 8),  
    `OUTPUT(Z, 16) //declare 16-bit output  
    `INOUT(F, 32) //declare 32-bit bidirectional port  
);  
<module body>  
endmodule
```

Instantiate sub-components

```
module my_module  
(  
  //module ports  
  ...  
);  
...  
  my_submodule comp0  
(  
    .X(A),  
    .Y(B),  
    .Z ( C),  
    .F (D)  
  )  
  ...  
endmodule
```


my_module

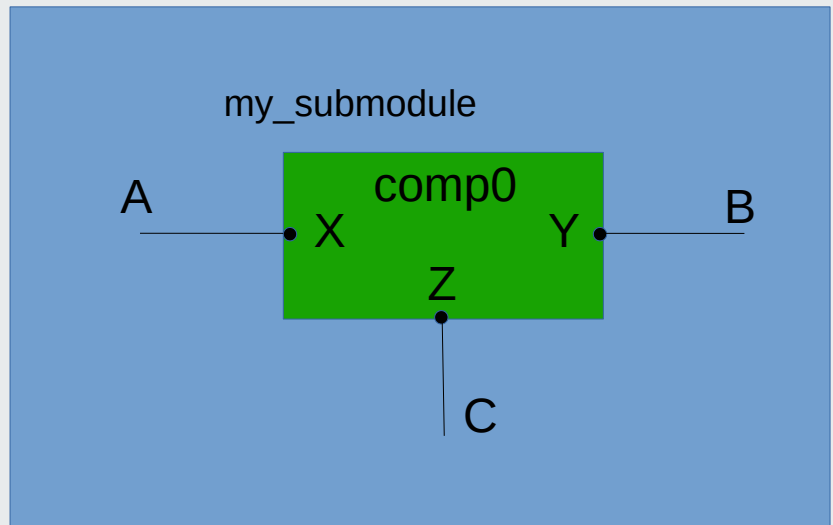


Wires and variables

- Circuits are blocks connected by wires that carry digital signals (0 or 1)
- So we need to declare and use wires
- Verilog describes two types of wires:
 - Type *wire*: used for connections and assign statements
 - Type *reg*: user for operation results within *always* and *initial* processes
- Using IOb Verilog macros:
 - Type wire: ``IOB_WIRE(NAME, WIDTH)`
 - Type reg: ``IOB_VAR(NAME, WIDTH)`
- Signed versions:
 - Type wire: ``IOB_WIRE_SIGNED(NAME, WIDTH)`
 - Type reg: ``IOB_VAR_SIGNED(NAME, WIDTH)`

 Typical module: combinatorial circuit plus register



IOb-lib: registers!

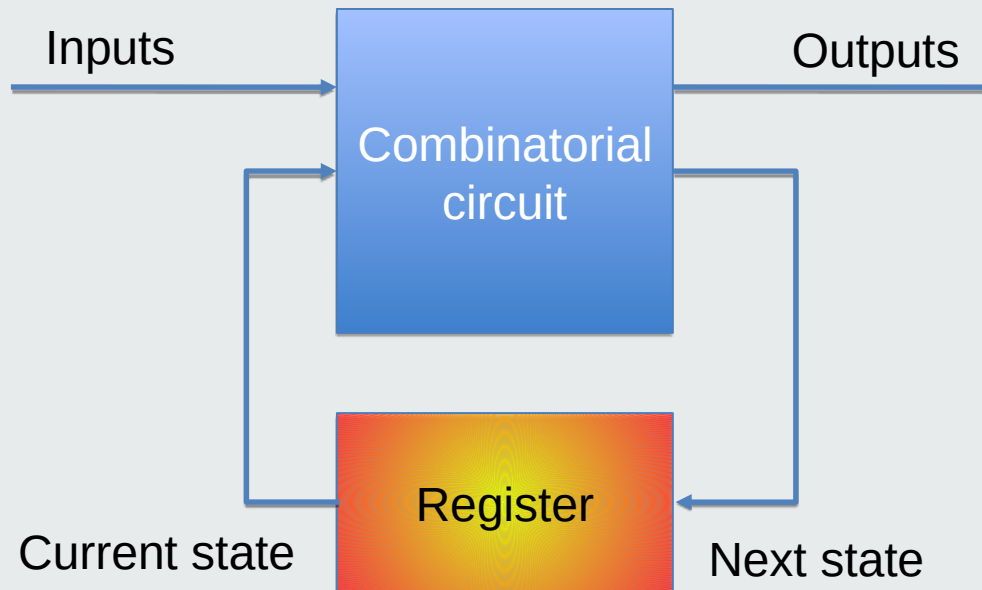

IOb-lib: registers

- IOb-lib users are not allowed to describe registers in Verilog (allowing tools to infer them)
- IOb-lib users must instantiate the `iob_reg` component

The iob_reg module

```
`timescale 1ns / 1ps
```

Exercise: instantiate a register


```
module iob_reg
#(
  parameter DATA_W = 0,
  parameter RST_VAL = 0
)
(
  input      clk,
  input      arst,
  input      rst,
  input      en,
  input [DATA_W-1:0] data_in,
  output reg [DATA_W-1:0] data_out
);

//prevent width mismatch
localparam [DATA_W-1:0] RST_VAL_INT = RST_VAL;

always @(posedge clk, posedge arst) begin
  if (arst) begin
    data_out <= RST_VAL_INT;
  end else if (rst) begin
    data_out <= RST_VAL_INT;
  end else if (en) begin
    data_out <= data_in;
  end
end

endmodule
```

IOb-lib: combinatorial circuits

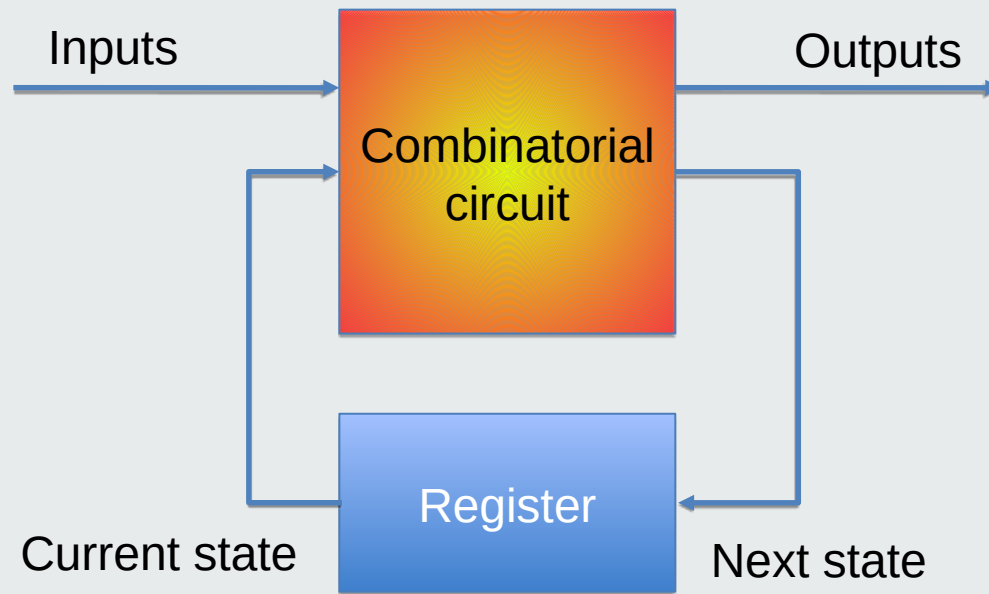

Combinatorial blocks

```
module my_module
(
  //interface signals
);
...
`IOB_VAR(zv,10);
`IOB_VAR(yv,10);
`IOB_COMB begin
  //insert C-like expressions here: examples
  zv = s? X: Y;
  yv = a*(b+c);
end
`IOB_VAR2WIRE(zv, z)
`IOB_VAR2WIRE(yv, y)
...
endmodule
```

WARNING: make sure you have
no feedback loops

`IOB_COMB is defined in iob_lib.vh:
`define IOB_COMB always @*

What is always @*?

The verilog explanation is
cumbersome

The **iob-lib** explanation is trivial:

- 1) `IOB_COMB describes a combinatorial block
- 2) LHS are computed variables using wires and other variables
- 3) RHS are inputs: wires or other variables
- 4) computed variables need to be converted to wires to be used for interconnection

Order of statements

- In Verilog the order of statements is **irrelevant** since we are merely listing components
- However:
 - Signal declarations must precede their use
 - Inside a combinatorial block, the order of statements is important because it is ***described procedurally***
 - Only the variables computed in a combinatorial block matters and this computation may be affected by the order of statements

Combinatorial block: if statements

```
module my_module
(
  //interface signals
);
...
  `IOB_VAR(zv,10);
  `IOB_COMB begin
    if (s)
      zv = x;
    else
      zv = y;
  end
  `IOB_VAR2WIRE(zv, z)
...
endmodule
```

```
module my_module
(
  //interface signals
);
...
  `IOB_VAR(zv,10);
  `IOB_COMB begin
    zv = y;
    if (s)
      zv = x;
  end
  `IOB_VAR2WIRE(zv, z)
...
endmodule
```

Combinatorial block: for loops

```
module my_module
(
  //interface signals
);
...
  integer i;
  `IOB_VAR(c,9);
  `IOB_VAR(s,8);
  `IOB_COMB begin

    for (i=0; i<N; i=i+1)
      s[i] = a[i] ^b[i] ^c[i];
      c[i+1] = a[i]&b[i] | ( c[i] & (a[i] ^b[i] ));
    end
  `IOB_VAR2WIRE(y, s)
  `IOB_VAR2WIRE(co, c[8])
...
endmodule
```